EXPERIMENT-4 REALIZATION OF MULTIPLEXERS AND DEMULTIPLEXERS


- **1. AIM:** To Design, simulate and implement Multiplexers and Demultiplexers in 2 different modeling styles(Data Flow, Structural Flow Modeling)
- 2. SOFTWARE USED: Xilinx Vivado 2022.2
- 3. PROCEDURE:
 - Open the Xilinx Vivado project navigator.
 - Open the Design source and go to add / create sources
 - Create new file, give appropriate name save it.
 - Open the file in the editor and write the Verilog code.
 - Open the Design source and go to add / create sources to create the test bench
 - Open the editor and write the Verilog code for test bench.
 - After completion of Verilog code set your test bench as top module in simulation settings and Run Simulation.
 - To view RTL schematic, select RTL Analysis in which select open elaborate design, select Schematic.

Multiplexers (Data Flow Modeling)

1.1 AIM: 2x1 Multiplexer [MUX]

1.2 SOFTWARE USED: Xilinx Vivado 2022.2

1.3 SYMBOL:

 

1.4 LOGIC EXPRESSION:

$$Y = ((\sim S)\&I_0) \mid (S)\&I_1))$$

1.5 BOOLEAN EXPRESSION:

$$\mathbf{Y} = \overline{\mathbf{S}}\mathbf{I}_0 + \mathbf{S}\mathbf{I}_1$$

1.6 TRUTH TABLE:

INPUT	OUTPUT
S	Y
0	$\mathbf{I_0}$
1	$\overline{\mathbf{I}}_{1}$

1.7 VERILOG CODE (Two_by_1_MUX_df.v):

$$\begin{split} & module \ Two_by_1_MUX_df(y,s,i); \\ & output \ y; \\ & input \ s; \\ & input[1:0]i; \\ & assign \ y = (((\sim\!s)\&i[0])|((s)\&i[1])); \\ & endmodule \end{split}$$

1.8 TEST BENCH (Two_by_1_MUX_df_tb.v):

```
module Two_by_1_MUX_df_tb();
reg s;
reg[1:0]i;
wire y;
Two_by_1_MUX_df x1(y,s,i);
initial
begin
s = 1'b0;i=2'b00;
#10 s = 1'b1;i=2'b01;

#10 s = 1'b1;i=2'b10;
#10 $finish;
end
endmodule
```

1.9 WAVEFORM:




1.10 RESULT:

2x1 Multiplexer is simulated and implemented in Data Flow Modeling.

1.1 AIM: 4x1 Multiplexer [MUX]

1.2 SOFTWARE USED: Xilinx Vivado 2022.2

1.3 SYMBOL:

 

1.4 LOGIC EXPRESSION:

$$Y = ((\sim\!S_0)\&\ (\sim\!S_1)\&I_0)\ |\ ((\sim\!S_0)\&\ (S_1)\&I_1)\ |\ ((S_0)\&\ (\sim\!S_1)\&I_2)\ |\ ((S_0)\&\ (S_1)\&I_3)$$

1.5 BOOLEAN EXPRESSION:

$$Y = \overline{S_0} \overline{S_1} I_0 + \overline{S_0} S_1 I_1 + S_0 \overline{S_1} I_2 + S_0 S_1 I_3$$

1.6 TRUTH TABLE:

INPUT		OUTPUT
$\mathbf{S_0}$	$\mathbf{S_1}$	Y
0	0	$\mathbf{I_0}$
0	1	I_1
1	0	\mathbf{I}_2
1	1	I_3


1.7 VERILOG CODE (MUX_4by1_df.v):

```
\label{eq:module MUX_4by1_df(y,s,i);} \\ \text{output } y; \\ \text{input } [1:0]s; \\ \text{input } [3:0]i; \\ \\ \text{assign } y = (\\ ((\sim s[0]) \& (\sim s[1]) \& (i[0]))| \\ ((\sim s[0]) \& (s[1]) \& (i[1]))| \\ ((s[0]) \& (\sim s[1]) \& (i[2]))| \\ ((s[0]) \& (s[1]) \& (i[3])) \\ ); \\ \text{endmodule} \\ \\ \\ \text{output } y; \\ \text
```

1.8 TEST BENCH (MUX_4by1_df_tb.v):

```
module MUX_4by1_df_tb();
reg [1:0]s;
reg[3:0]i;
wire y;
MUX_4by1_df x1(y,s,i);
initial
begin
s = 2'b00; i=4'b0000;
#10 s = 2'b00; i=4'b0001;
#10 s = 2'b01; i=4'b0000;
#10 s = 2'b01; i=4'b0010;
#10 s = 2'b10; i=4'b0000;
#10 s = 2'b10; i=4'b0100;
#10 s = 2'b11;i=4'b0000;
#10 s = 2'b11;i=4'b1000;
#10 $finish;
end
```

endmodule **1.9 WAVEFORM:**

 


1.10 RESULT:

4x1 Multiplexer is simulated and implemented in Data Flow Modeling.

1.1 AIM: 8x1 Multiplexer [MUX]

1.2 SOFTWARE USED: Xilinx Vivado 2022.2

1.3 SYMBOL:

 

1.4 LOGIC EXPRESSION:

$$\begin{split} Y = & ((\sim & S_0) \ \& \ (\sim & S_1) \ \& \ (\sim & S_2) \ \& \ (\sim & S_3) \ \& \ I_0) \ | \\ & ((\sim & S_0) \ \& \ (\sim & S_1) \ \& \ (\sim & S_2) \ \& \ (S_3) \ \& \ I_1) \ | \\ & ((\sim & S_0) \ \& \ (\sim & S_1) \ \& \ (S_2) \ \& \ (\sim & S_3) \ \& I_2) \ | \\ & ((\sim & S_0) \ \& \ (\sim & S_1) \ \& \ (S_2) \ \& \ (\sim & S_3) \ \& I_3) \ | \\ & ((\sim & S_0) \ \& \ (S_1) \ \& \ (\sim & S_2) \ \& \ (\sim & S_3) \ \& I_4) \ | \\ & ((\sim & S_0) \ \& \ (S_1) \ \& \ (\sim & S_2) \ \& \ (\sim & S_3) \ \& I_5) \ | \\ & ((\sim & S_0) \ \& \ (S_1) \ \& \ (S_2) \ \& \ (\sim & S_3) \ \& I_6) \ | \\ & ((\sim & S_0) \ \& \ (S_1) \ \& \ (S_2) \ \& \ (S_3) \ \& I_7) \end{split}$$

1.5 BOOLEAN EXPRESSION:

$$Y = \overline{S_0} \overline{S_1} \overline{S_2} \overline{S_3} I_0 + \overline{S_0} \overline{S_1} \overline{S_2} S_3 I_1 + \overline{S_0} \overline{S_1} S_2 \overline{S_3} I_2 + \overline{S_0} \overline{S_1} S_2 S_3 I_3 + \overline{S_0} S_1 \overline{S_2} \overline{S_3} I_4 + \overline{S_0} \overline{S_1} \overline{S_2} \overline{S_3} I_5 + \overline{S_0} \overline{S_1} S_2 \overline{S_3} I_6 + \overline{S_0} \overline{S_1} S_2 \overline{S_3} I_7 + \overline{S_0} \overline{S_1} \overline{S_2} \overline{S_3} I_7 + \overline{S_0} \overline{S_1} \overline{S_1}$$

1.6 TRUTH TABLE:

INPUT			OUTPUT	
S_0	S_1	S_2	S_3	I
0	0	0	0	$\mathbf{I_0}$
0	0	0	1	I_1
0	0	1	0	\mathbf{I}_2
0	0	1	1	I_3
0	1	0	0	I_4
0	1	0	1	I_5
0	1	1	0	I_6
0	1	1	1	\mathbf{I}_7

```
1.7 VERILOG CODE (MUX_8by1_df.v):
    module MUX_8by1_df(y,s,i);
    output y;
    input [3:0]s;
    input[7:0]i;
    assign y = (
    ((\sim s[0])\&(\sim s[1])\&(\sim s[2])\&(\sim s[3])\&(i[0]))
    ((\sim s[0])\&(\sim s[1])\&(\sim s[2])\&(s[3])\&(i[1]))
    ((\sim s[0])\&(\sim s[1])\&(s[2])\&(\sim s[3])\&(i[2]))
    ((\sim s[0])\&(\sim s[1])\&(s[2])\&(s[3])\&(i[3]))
    ((\sim s[0])\&(s[1])\&(\sim s[2])\&(\sim s[3])\&(i[4]))
    ((\sim s[0])\&(s[1])\&(\sim s[2])\&(s[3])\&(i[5]))
    ((\sim s[0])\&(s[1])\&(s[2])\&(\sim s[3])\&(i[6]))
    ((\sim s[0])\&(s[1])\&(s[2])\&(s[3])\&(i[7]))
    );
    endmodule.
1.8 TEST BENCH (MUX_8by1_df_tb.v):
    module MUX_8by1_df_tb();
    reg [3:0]s;
    reg[7:0]i;
    wire y;
    MUX_8by1_df x1(y,s,i);
    initial
    begin
    s = 4'b0000;i=8'b00000000;
    #10 s = 4'b0000; i=8'b00000001;
    #10 s = 4'b0001; i=8'b000000000;
    #10 s = 4'b0001; i=8'b00000010;
    #10 s = 4'b0010; i=8'b000000000;
    #10 s = 4'b0010; i=8'b00000100;
    #10 s = 4'b0011; i=8'b000000000;
    #10 s = 4'b0011; i=8'b00001000;
    #10 s = 4'b0100;i=8'b000000000;
    #10 s = 4'b0100;i=8'b00010000;
    #10 s = 4'b0101; i=8'b000000000;
    #10 s = 4'b0101;i=8'b00100000;
    #10 s = 4'b0110; i=8'b000000000;
    #10 s = 4'b0110;i=8'b01000000;
```


```
#10 s = 4'b0111;i=8'b00000000;
#10 s = 4'b0111;i=8'b10000000;
```

#10 \$finish;

end

endmodule

1.9 WAVEFORM:

 

1.10 RESULT:


8x1 Multiplexer is simulated and implemented in Data Flow Modeling.

Multiplexers (Structural Flow Modeling)

1.1 AIM: 2x1 Multiplexer [MUX]

1.2 SOFTWARE USED: Xilinx Vivado 2022.2

1.3 SYMBOL:

 

1.4 LOGIC EXPRESSION:

$$Y = ((\sim S)\&I_0) \mid (S)\&I_1))$$

1.5 BOOLEAN EXPRESSION:

$$Y = \overline{S}I_0 + SI_1$$

1.6 TRUTH TABLE:

INPUT	OUTPUT	
S	Y	
0	$\mathbf{I_0}$	
1	I_1	

1.7 VERILOG CODE (MUX_2by1_sf.v):

 $module\ MUX_2by1_sf(y,s,i);$

output y;

input s;

input[1:0]i;

wire a,b,c;

and $(a, \sim s, i[0]);$

and (b,s,i[1]);

or(y,a,b);

endmodule

1.8 TEST BENCH (MUX_2by1_sf_tb.v):

```
module MUX_2by1_sf_tb();
reg s;
reg[1:0]i;
wire y;

MUX_2by1_sf x1(y,s,i);
initial
begin
s = 1'b0;i=2'b00;
#10 s = 1'b0;i=2'b01;

#10 s = 1'b1;i=2'b00;
#10 s = 1'b1;i=2'b10;

#10 $finish;
end
```

endmodule **1.9 WAVEFORM:**




1.10 RESULT:

2x1 Multiplexer is simulated and implemented in Structural Flow Modeling.

1.1 AIM: 4x1 Multiplexer [MUX]

1.2 SOFTWARE USED: Xilinx Vivado 2022.2

1.3 SYMBOL:

 

1.4 LOGIC EXPRESSION:

$$Y = ((\sim\!S_0)\&\ (\sim\!S_1)\&I_0)\ |\ ((\sim\!S_0)\&\ (S_1)\&I_1)\ |\ ((S_0)\&\ (\sim\!S_1)\&I_2)\ |\ ((S_0)\&\ (S_1)\&I_3)$$

1.5 BOOLEAN EXPRESSION:

$$Y = \overline{S_0} \overline{S_1} I_0 + \overline{S_0} S_1 I_1 + S_0 \overline{S_1} I_2 + S_0 S_1 I_3$$

1.6 TRUTH TABLE:

INPUT		OUTPUT
$\mathbf{S_0}$	$\mathbf{S_1}$	Y
0	0	$\mathbf{I_0}$
0	1	I_1
1	0	I_2
1	1	I_3

1.7 VERILOG CODE (MUX_4by1_sf.v):

module MUX_4by1_sf(y,s,i);

output y;

input [1:0]s;

input[3:0]i;

wire a1,a2,b1,b2,c1,c2,d1,d2,o1,o2;


and $(a1, \sim s[0], \sim s[1]);$

and (a2,a1,i[0]);

and $(b1, \sim s[0], s[1]);$

```
and (b2,b1,i[1]);
   and (c1,s[0],\sim s[1]);
   and (c2,c1,i[2]);
   and (d1,s[0],s[1]);
   and (d2,d1,i[3]);
   or (o1,a2,b2);
   or (o2.c2,d2);
   or (y,o1,o2);
   endmodule
1.8 TEST BENCH (MUX_4by1_sf_tb.v):
   module MUX_4by1_sf_tb();
   reg [1:0]s;
   reg[3:0]i;
   wire y;
   MUX_4by1_sf x1(y,s,i);
   initial
   begin
   s = 2'b00; i=4'b0000;
   #10 s = 2'b00; i=4'b0001;
   #10 s = 2'b01; i=4'b0000;
   #10 s = 2'b01; i=4'b0010;
   #10 s = 2'b10;i=4'b0000;
   #10 s = 2'b10;i=4'b0100;
   #10 s = 2'b11;i=4'b0000;
   #10 s = 2'b11;i=4'b1000;
   #10 $finish;
   end
   endmodule
```

1.9 WAVEFORM:

 


1.10 RESULT:

4x1 Multiplexer is simulated and implemented in Structural Flow Modeling.

1.1 AIM: 8x1 Multiplexer [MUX]

1.2 SOFTWARE USED: Xilinx Vivado 2022.2

1.3 SYMBOL:

 

1.4 LOGIC EXPRESSION:

$$\begin{split} Y = & ((\sim & S_0) \ \& \ (\sim & S_1) \ \& \ (\sim & S_2) \ \& \ (\sim & S_3) \ \& \ I_0) \ | \\ & ((\sim & S_0) \ \& \ (\sim & S_1) \ \& \ (\sim & S_2) \ \& \ (S_3) \ \& \ I_1) \ | \\ & ((\sim & S_0) \ \& \ (\sim & S_1) \ \& \ (S_2) \ \& \ (\sim & S_3) \ \& I_2) \ | \\ & ((\sim & S_0) \ \& \ (\sim & S_1) \ \& \ (S_2) \ \& \ (S_3) \ \& I_3) \ | \\ & ((\sim & S_0) \ \& \ (S_1) \ \& \ (\sim & S_2) \ \& \ (\sim & S_3) \ \& I_4) \ | \\ & ((\sim & S_0) \ \& \ (S_1) \ \& \ (\sim & S_2) \ \& \ (\sim & S_3) \ \& I_5) \ | \\ & ((\sim & S_0) \ \& \ (S_1) \ \& \ (S_2) \ \& \ (\sim & S_3) \ \& I_6) \ | \\ & ((\sim & S_0) \ \& \ (S_1) \ \& \ (S_2) \ \& \ (S_3) \ \& I_7) \end{split}$$

1.5 BOOLEAN EXPRESSION:

$$Y = \overline{S_0S_1S_2S_3I_0} + \overline{S_0S_1S_2S_3I_1} + \overline{S_0S_1S_2S_3I_2} + \overline{S_0S_1S_2S_3I_3} + \overline{S_0S_1S_2S_3I_4} + \overline{S_0S_1S_2S_3I_5} + \overline{S_0S_1S_2S_3I_6} + \overline{S_0S_1S_2S_3I_7} + \overline{S_0S_1S_2S_3I_6} + \overline{S_0S_1S_2S_3I_7} + \overline{S_0S_1S_2S_3I_6} + \overline{S_0S_1S_2S_3I_7} + \overline{S_0S_1S_2S_3I_6} + \overline{S_0S_1S_2S_3I_7} + \overline{S_0S_1S_2S_2S_3I_7} + \overline{S_0S_1S_2S_2S_3I_7} + \overline{S_0S_1S_2S_2S_3I_7} + \overline{S_0S_1S_2S_2S_2S_2S_2S_2S_2S_2S_2S$$

1.6 TRUTH TABLE:

INPUT			OUTPUT	
S_0	S_1	S_2	S_3	I
0	0	0	0	$\mathbf{I_0}$
0	0	0	1	I_1
0	0	1	0	I_2
0	0	1	1	I_3
0	1	0	0	I_4
0	1	0	1	I_5
0	1	1	0	I_6
0	1	1	1	I_7

1.7 VERILOG CODE (MUX_8by1_sf.v):

```
module MUX_8by1_sf(y,s,i);
output y;
input [3:0]s;
input [7:0]i;
wire a1,a2,a3,a4;
wire b1,b2,b3,b4;
wire c1,c2,c3,c4;
wire d1,d2,d3,d4;
wire e1,e2,e3,e4;
wire f1,f2,f3,f4;
wire g1,g2,g3,g4;
wire h1,h2,h3,h4;
wire o1,o2,o3,o4;
wire y1,y2;
and (a1, \sim s[0], \sim s[1]);
and (a2, \sim s[2], \sim s[3]);
and(a3,a1,a2);
and(a4,a3,i[0]);
and (b1, \sim s[0], \sim s[1]);
and (b2,~s[2],s[3]);
and (b3,b1,b2);
and (b4,b3,i[1]);
and (c1, \sim s[0], \sim s[1]);
and (c2,s[2],\sim s[3]);
and (c3,c1,c2);
and (c4,c3,i[2]);
and (d1, \sim s[0], \sim s[1]);
and (d2,s[2],s[3]);
and (d3,d1,d2);
and (d4,d3,i[3]);
and (e1, \sim s[0], s[1]);
and (e2, \sim s[2], \sim s[3]);
and (e3,e1,e2);
and (e4,e3,i[4]);
and (f1, \sim s[0], s[1]);
and (f2, \sim s[2], s[3]);
and (f3,f1,f2);
and (f4,f3,i[5]);
```


and $(g1, \sim s[0], s[1]);$

```
and (g2,s[2],\sim s[3]);
   and (g3,g1,g2);
   and (g4,g3,i[6]);
   and (h1, \sim s[0], s[1]);
   and (h2,s[2],s[3]);
   and (h3,h1,h2);
   and (h4,h3,i[7]);
   or (o1,a4,b4);
   or (o2,c4,d4);
   or (o3,e4,f4);
   or (o4,g4,h4);
   or(y1,o1,o2);
   or(y2,o3,o4);
   or(y,y1,y2);
   endmodule
1.8 TEST BENCH (MUX_8by1_sf_tb.v):
   module MUX_8by1_sf_tb();
   reg [3:0]s;
   reg[7:0]i;
   wire y;
   MUX_8by1_sf x1(y,s,i);
   initial
   begin
   s = 4'b0000; i=8'b00000000;
   #10 s = 4'b0000; i=8'b00000001;
   #10 s = 4'b0001; i=8'b00000000;
   #10 s = 4'b0001; i=8'b00000010;
   #10 s = 4'b0010;i=8'b00000000;
   #10 s = 4'b0010;i=8'b00000100;
   #10 s = 4'b0011;i=8'b00000000;
   #10 s = 4'b0011;i=8'b00001000;
   #10 s = 4'b0100;i=8'b00000000;
   #10 s = 4'b0100;i=8'b00010000;
   #10 s = 4'b0101;i=8'b000000000;
   #10 s = 4'b0101;i=8'b00100000;
```

LOGIC DESIGN LAB

```
#10 s = 4'b0110;i=8'b00000000;
#10 s = 4'b0110;i=8'b01000000;
#10 s = 4'b0111;i=8'b000000000;
#10 s = 4'b0111;i=8'b100000000;
#10 $finish;
end
endmodule
```

1.9 WAVEFORM:

 

1.10 RESULT:


8x1 Multiplexer is simulated and implemented in Structural Flow Modeling.

LOGIC DESIGN LAB

1.1 AIM: 4x1 MUX using 2x1 MUX

1.2 SOFTWARE USED: Xilinx Vivado 2022.2

1.3 SYMBOL:

 

1.4 LOGIC EXPRESSION:

$$Y = ((-S_0)\&\ (-S_1)\&I_0)\ |\ ((-S_0)\&\ (S_1)\&I_1)\ |\ ((S_0)\&\ (-S_1)\&I_2)\ |\ ((S_0)\&\ (S_1)\&I_3)$$

1.5 BOOLEAN EXPRESSION:

$$Y = \overline{S_0}\overline{S_1}I_0 + \overline{S_0}S_1I_1 + S_0\overline{S_1}I_2 + S_0S_1I_3$$

1.6 TRUTH TABLE:

INPUT		OUTPUT
S_0	S_1	Y
0	0	$\mathbf{I_0}$
0	1	\mathbf{I}_1
1	0	I_2
1	1	I_3

1.7 VERILOG CODE (MUX_4by1_using_2by1_MUX.v):

module MUX_4by1_using_2by1_MUX(y,s,i);

input [3:0]i;

input [1:0]s;

output y;

wire [1:0]w;

MUX 2by1 sf m1(w[0],s[0],i[1:0]);

MUX_2by1_sf m2(w[1],s[0],i[3:2]);

MUX_2by1_sf m3(y,s[1],w[1:0]);

endmodule


1.8 TEST BENCH (MUX_4by1_using_2by1_MUX _tb.v):

```
module MUX_4by1_using_2by1_MUX_tb();
reg [1:0]s;
reg[3:0]i;
wire y;
MUX_4by1_using_2by1_MUX x1(y,s,i);
initial
begin
s = 2'b00; i=4'b0000;
#10 s = 2'b00; i=4'b0001;
#10 s = 2'b01; i=4'b0000;
#10 s = 2'b01;i=4'b0010;
#10 s = 2'b10;i=4'b0000;
#10 s = 2'b10;i=4'b0100;
#10 s = 2'b11; i=4'b0000;
#10 s = 2'b11;i=4'b1000;
#10 $finish;
```

end

endmodule

1.9 WAVEFORM:

 

1.10 RESULT:

4x1 Multiplexer is simulated and implemented using 2x1 Multiplexer.