

EXPERIMENT-2

REALIZATION OF ADDERS AND SUBTRACTORS (HALF, FULL)


1. **AIM:** To Design, simulate and implement Adders and Subtractors in 3 different modeling styles(Data Flow, Behavioral Flow, Structural Flow Modeling)
2. **SOFTWARE USED:** Xilinx Vivado 2022.2
3. **PROCEDURE:**
 - Open the Xilinx Vivado project navigator.
 - Open the Design source and go to add / create sources
 - Create new file, give appropriate name save it.
 - Open the file in the editor and write the Verilog code.
 - Open the Design source and go to add / create sources to create the test bench
 - Open the editor and write the Verilog code for test bench.
 - After completion of Verilog code set your test bench as top module in simulation settings and Run Simulation.
 - To view RTL schematic, select RTL Analysis in which select open elaborate design, select Schematic.

ADDERS (Data Flow Modeling)

1.1 AIM: To implement Half Adder

1.2 SOFTWARE USED: Xilinx Vivado 2022.2

1.3 SYMBOL:

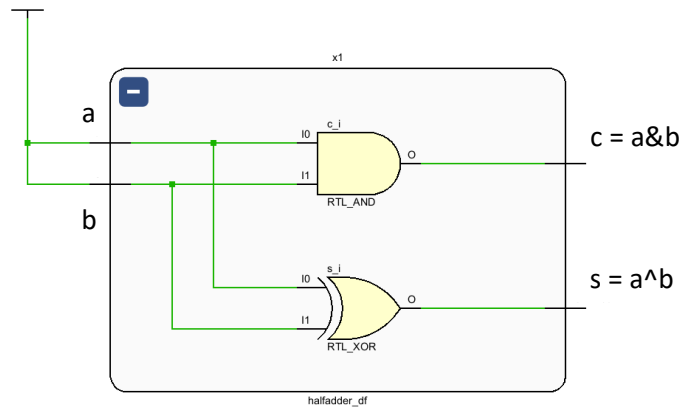

1.4 LOGIC EXPRESSION:

$$S = A \oplus B$$

$$C = A \& B$$

1.5 BOOLEAN EXPRESSION:

$$S = \bar{A}B + A\bar{B}$$

$$C = A.B$$

1.6 TRUTH TABLE:

INPUT		OUTPUT	
A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

1.7 VERILOG CODE (halfadder_df.v):


```

module halfadder_df(s,c,a,b);
    output s,c;
    input a,b;
    assign s = a^b;
    assign c = a&b;
endmodule
    
```

1.8 TEST BENCH (halfadder_df_tb.v):

```
module halfadder_df_tb();
    reg a,b;
    wire s,c;
    halfadder_df x1(s,c,a,b);
    initial
    begin
        {a,b}=2'b00;
        #10 {a,b}=2'b01;
        #20 {a,b}=2'b10;
        #40 {a,b}=2'b11;
        #60 $finish;
    end
endmodule
```

1.9 WAVEFORM:

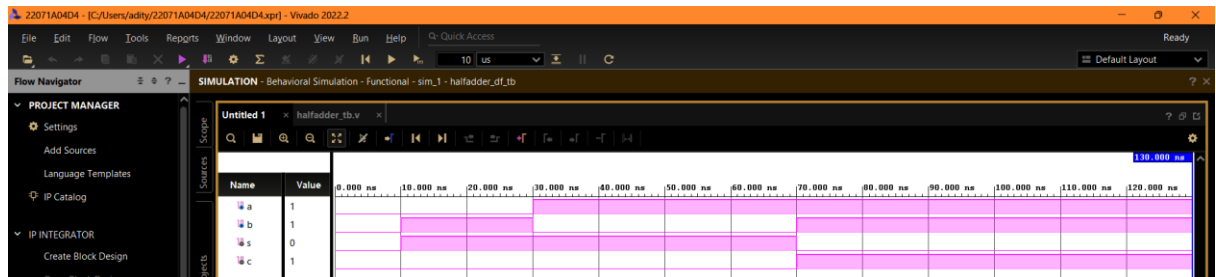

1.10 OBSERVATION:

In half adder, the sum of the two inputs is represented using logical XOR Gate and carry is represented using logical AND Gate.


1.11 RESULT:

Half Adder is simulated and implemented in Data Flow Modeling.

2.1 AIM: To implement Full Adder

2.2 SOFTWARE USED: Xilinx Vivado 2022.2

2.3 SYMBOL:

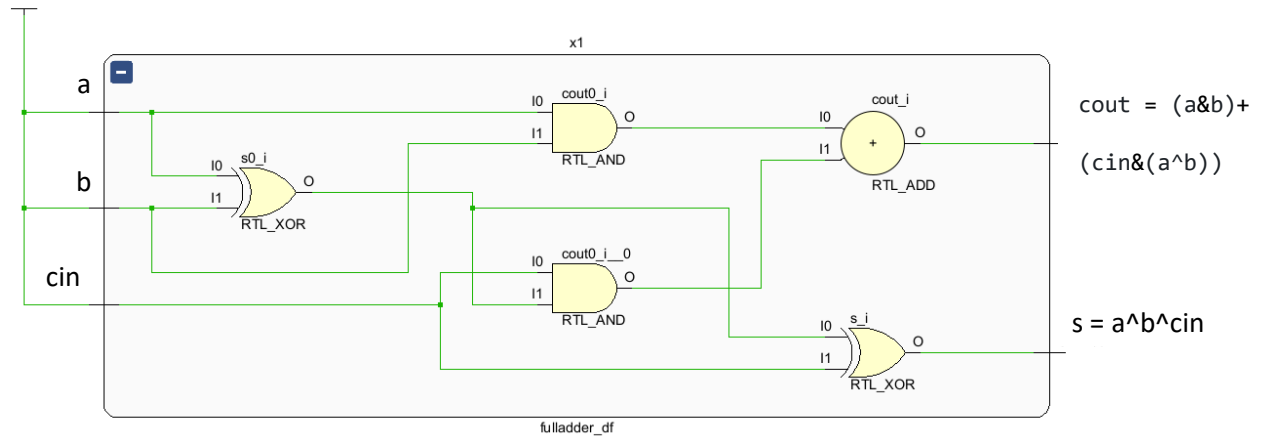

2.4 LOGIC EXPRESSION:

$$S = A \oplus B \oplus \text{Cin}$$

$$C = (A \& B) + (\text{Cin} \& (A \oplus B))$$

2.5 BOOLEAN EXPRESSION:

$$S = \overline{A}(\overline{B}\text{Cin} + B\overline{\text{Cin}}) + A(\overline{B}\text{Cin} + B\overline{\text{Cin}})$$

$$C = AB + \text{Cin}(\overline{A}B + A\overline{B})$$

2.1 TRUTH TABLE:

INPUT			OUTPUT	
A	B	Cin	S	C
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

2.2 VERILOG CODE (fulladder_df.v):

```


module fulladder_df(s,cout,a,b,cin);
output s,cout;
input a,b,cin;
assign s = a^b^cin;
assign cout = (a&b)+(cin&(a^b));
endmodule
    
```

2.3 TEST BENCH (fulladder_df_tb.v):

```

module fulladder_df_tb();
reg a,b,cin;
wire s,cout;
fulladder_df x1(s,cout,a,b,cin);
initial
begin
    {a,b,cin}=3'b000;
    #10 {a,b,cin}=3'b001;
    #10 {a,b,cin}=3'b010;
    #10 {a,b,cin}=3'b011;
    #10 {a,b,cin}=3'b100;
    #10 {a,b,cin}=3'b101;
    #10 {a,b,cin}=3'b110;
    #10 {a,b,cin}=3'b111;
end
endmodule
    
```

2.4 WAVEFORM:

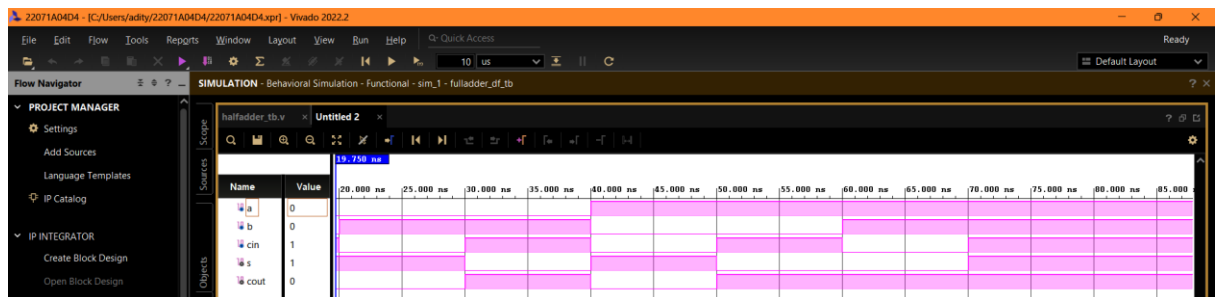


2.5 OBSERVATION:

In full adder, the sum of the two inputs is represented using $S = A \oplus B \oplus Cin$ and carry is represented using $C = (A \& B) + (Cin \& (A \oplus B))$

2.6 RESULT:

Full Adder is simulated and implemented in Data Flow Modeling.

 ADDERS (Behavioral Flow Modeling)**1.1 AIM:** To implement Half Adder**1.2 SOFTWARE USED:** Xilinx Vivado 2022.2**1.3 SYMBOL:****1.4 LOGIC EXPRESSION:**

$$S = A \oplus B$$

$$C = A \& B$$

1.5 BOOLEAN EXPRESSION:

$$S = \bar{A}B + A\bar{B}$$

$$C = A.B$$

1.6 TRUTH TABLE:

INPUT		OUTPUT	
A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

1.7 VERILOG CODE (halfadder_bf.v):

```
module halfadder_bf(s,c,a,b);
```

```
output s,c;
```

```
input a,b;
```

```
reg s,c;
```

```
always @(a,b)
```

```
begin
```

```
if(a==1'b0 & b==1'b0)
```

```
begin
```

```
s=0;
```

```
c=0;
```

```
end
```

```
else if(a==1'b0 & b==1'b1)
```


```
begin
s=1;
c=0;
end

else if(a==1'b1 & b==1'b0)
begin
s=1;
c=0;
end
else if(a==1'b1 & b==1'b1)
begin
s=0;
c=1;
end
end
endmodule
```

1.8 TEST BENCH (halfadder_bf_tb.v):

```
module halfadder_bf_tb();
reg a,b;
wire s,c;
halfadder_bf x1(s,c,a,b);
initial
begin
{a,b}=2'b00;
#10 {a,b}=2'b01;
#20 {a,b}=2'b10;
#40 {a,b}=2'b11;
#60 $finish;
end
endmodule
```

1.9 WAVEFORM:

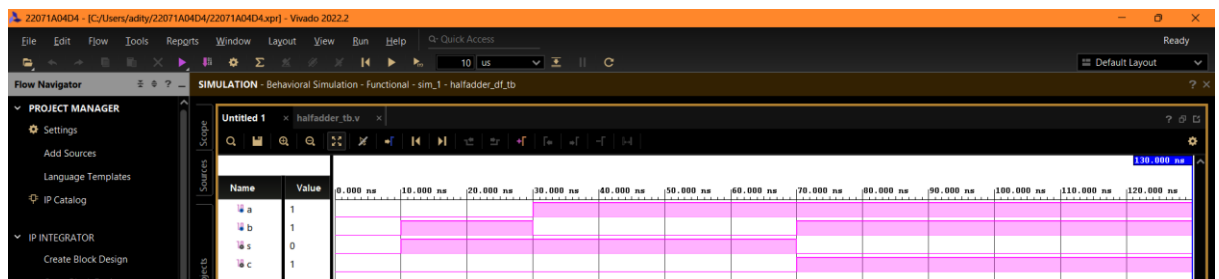

1.10 OBSERVATION:

In half adder, the sum of the two inputs is represented using logical XOR Gate and carry is represented using logical AND Gate.


1.11 RESULT:

Half Adder is simulated and implemented in Behavioral Flow Modeling.

2.1 AIM: To implement Full Adder

2.2 SOFTWARE USED: Xilinx Vivado 2022.2

2.3 SYMBOL:

 

2.4 LOGIC EXPRESSION:

$$S = A \oplus B \oplus \text{Cin}$$

$$C = (A \& B) + (\text{Cin} \& (A \oplus B))$$

2.5 BOOLEAN EXPRESSION:

$$S = \overline{A}(B\text{Cin} + \overline{B}\overline{\text{Cin}}) + A(\overline{B}\text{Cin} + B\overline{\text{Cin}})$$

$$C = AB + \text{Cin}(\overline{A}B + A\overline{B})$$

2.6 TRUTH TABLE:

INPUT			OUTPUT	
A	B	Cin	S	C
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

2.7 VERILOG CODE (fulladder_bf.v):

```

module fulladder_bf(s,cout,a,b,cin);
    output s,cout;
    input a,b,cin;
    reg s,cout;
    always@(a,b,cin)
    begin
        if(a==1'b0 & b==1'b0 & cin==1'b0)
            begin
                s=0;
                cout = 0;
            end
    end


```



```
    else if(a==1'b0 & b==1'b0 & cin==1'b1)
        begin
            s=1;
            cout = 0;
        end
    else if(a==1'b0 & b==1'b1 & cin==1'b0)
        begin
            s=1;
            cout = 0;
        end
    else if(a==1'b0 & b==1'b1 & cin==1'b1)
        begin
            s=0;
            cout = 1;
        end
    else if(a==1'b1 & b==1'b0 & cin==1'b0)
        begin
            s=1;
            cout = 0;
        end
    else if(a==1'b1 & b==1'b0 & cin==1'b1)
        begin
            s=0;
            cout = 1;
        end
    else if(a==1'b1 & b==1'b1 & cin==1'b0)
        begin
            s=0;
            cout = 1;
        end
    else if(a==1'b1 & b==1'b1 & cin==1'b1)
        begin
            s=1;
            cout = 1;
        end
    else
        begin
            s=0;
            cout = 0;
        end
end
endmodule
```

2.8 TEST BENCH (fulladder_df_tb.v):


```
module fulladder_df_tb();
    reg a,b,cin;
    wire s,cout;
    fulladder_df x1(s,cout,a,b,cin);
    initial
    begin
        {a,b,cin}=3'b000;
        #10 {a,b,cin}=3'b001;
        #10 {a,b,cin}=3'b010;
        #10 {a,b,cin}=3'b011;
        #10 {a,b,cin}=3'b100;
        #10 {a,b,cin}=3'b101;
        #10 {a,b,cin}=3'b110;
        #10 {a,b,cin}=3'b111;
    end
endmodule
```

 2.9 WAVEFORM:**2.10 OBSERVATION:**

In full adder, the sum of the two inputs is represented using $S = A \oplus B \oplus Cin$ and carry is represented using $C = (A \& B) + (Cin \& (A \oplus B))$

2.11 RESULT:

Full Adder is simulated and implemented in Behavioral Flow Modeling.

 ADDERS (Structural Flow Modeling)**1.1 AIM:** To implement Half Adder**1.2 SOFTWARE USED:** Xilinx Vivado 2022.2**1.3 SYMBOL:****1.4 LOGIC EXPRESSION:**

$$S = A \oplus B$$

$$C = A \& B$$

1.5 BOOLEAN EXPRESSION:

$$S = \bar{A}B + A\bar{B}$$

$$C = A.B$$

1.6 TRUTH TABLE:

INPUT		OUTPUT	
A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

1.7 VERILOG CODE (halfadder_sf.v):

```

module halfadder_sf(s,c,a,b);
    output s,c;
    input a,b;
    wire s,c;
    xor (s,a,b);
    and (c,a,b);
endmodule

```

1.8 TEST BENCH (halfadder_sf_tb.v):


```

module halfadder_sf_tb();
    reg a,b;
    wire s,c;
    halfadder_sf x1(s,c,a,b);

```

```
initial
begin
{a,b}=2'b00;
#10 {a,b}=2'b01;
#20 {a,b}=2'b10;
#40 {a,b}=2'b11;
#60 $finish;
end
endmodule
```

1.9 WAVEFORM:

 

1.10 OBSERVATION:

In half adder, the sum of the two inputs is represented using logical XOR Gate and carry is represented using logical AND Gate.


1.11 RESULT:

Half Adder is simulated and implemented in Structural Flow Modeling.

2.1 AIM: To implement Full Adder

2.2 SOFTWARE USED: Xilinx Vivado 2022.2

2.3 SYMBOL:

 

2.4 LOGIC EXPRESSION:

$$S = A \oplus B \oplus \text{Cin}$$

$$C = (A \& B) + (\text{Cin} \& (A \& B))$$

2.5 BOOLEAN EXPRESSION:

$$S = \overline{A}(\overline{B}\text{Cin} + B\overline{\text{Cin}}) + A(\overline{B}\text{Cin} + B\overline{\text{Cin}})$$

$$C = AB + \text{Cin}(\overline{A}B + A\overline{B})$$

2.6 TRUTH TABLE:

INPUT			OUTPUT	
A	B	Cin	S	C
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

2.7 VERILOG CODE (fulladder_sf.v):

```

module fulladder_sf(s,cout,a,b,cin);
    output s,cout;
    input a,b,cin;
    wire w,x,y,z;
    xor (w,a,b);
    xor(s,w,cin);


```

```
and (x,a,b);
xor (y,a,b);
and (z,cin,y);
or (cout,x,z);
endmodule
```

2.8 TEST BENCH (fulladder_sf_tb.v):

```
module fulladder_sf_tb();
reg a,b,cin;
wire s,cout;
fulladder_sf x1(s,cout,a,b,cin);
initial
begin
    {a,b,cin}=3'b000;
    #10 {a,b,cin}=3'b001;
    #10 {a,b,cin}=3'b010;
    #10 {a,b,cin}=3'b011;
    #10 {a,b,cin}=3'b100;
    #10 {a,b,cin}=3'b101;
    #10 {a,b,cin}=3'b110;
    #10 {a,b,cin}=3'b111;
end
endmodule
```

2.9 WAVEFORM:

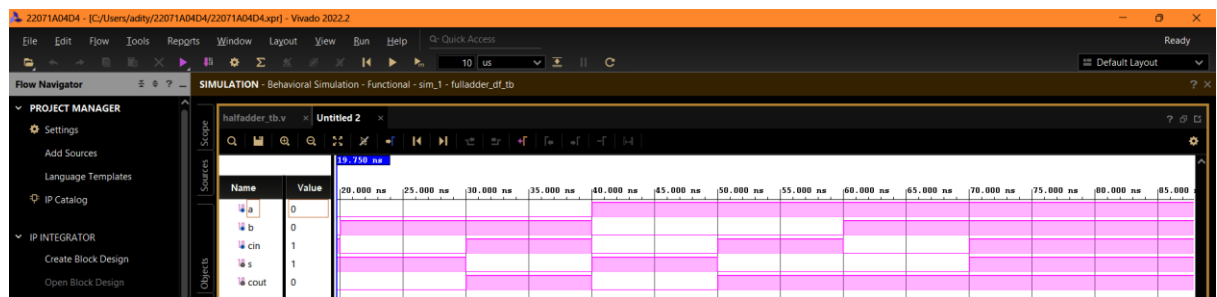

2.10 OBSERVATION:

In full adder, the sum of the two inputs is represented using $S = A \oplus B \oplus Cin$ and carry is represented using $C = (A \& B) + (Cin \& (A \oplus B))$

2.11 RESULT:


Full Adder is simulated and implemented in Structural Flow Modeling.

SUBTRACTORS (Data Flow Modeling)

1.1 AIM: To implement Half Subtractor

1.2 SOFTWARE USED: Xilinx Vivado 2022.2

1.3 SYMBOL:

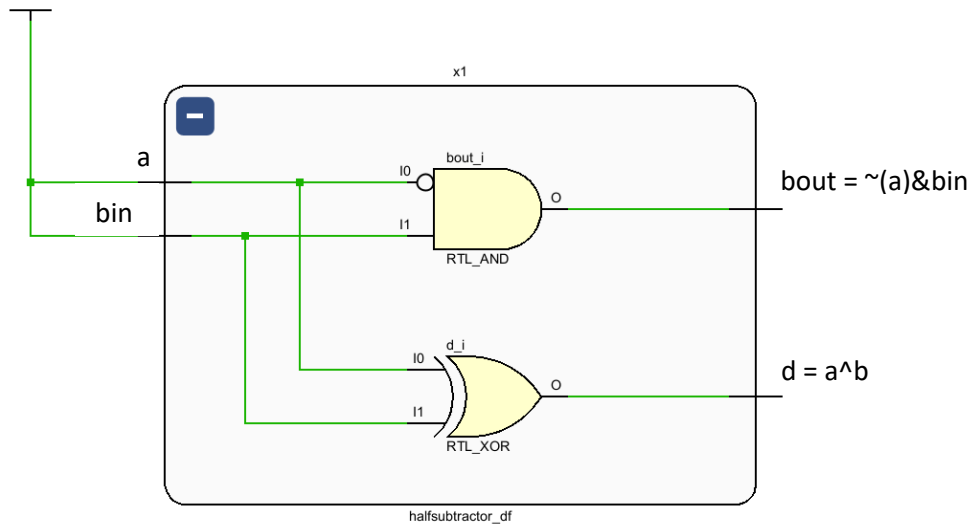

1.4 LOGIC EXPRESSION:

$$D = A \oplus \text{Bin}$$

$$\text{Bout} = \sim(A) \& \text{Bin}$$

1.5 BOOLEAN EXPRESSION:

$$S = \bar{A}\text{Bin} + A\bar{\text{Bin}}$$

$$\text{Bout} = \bar{A}.B$$

1.6 TRUTH TABLE:

INPUT		OUTPUT	
A	Bin	D	Bout
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0


1.7 VERILOG CODE (halfsubtractor_df.v):

```
module halfsubtractor_df(d,bout,a,bin);
    output d,bout;
    input a,bin;
    assign d = a^bin;
    assign bout = ~(a)&bin;
endmodule
```

1.8 TEST BENCH (halfsubtractor_df_tb.v):

```
module halfsubtractor_df_tb();  
    reg a,bin;  
    wire d,bout;  
    halfsubtractor_df x1(d,bout,a,bin);  
    initial  
    begin  
        {a,bin}=2'b00;  
        #10 {a,bin}=2'b01;  
        #20 {a,bin}=2'b10;  
        #40 {a,bin}=2'b11;  
        #60 $finish;  
    end  
endmodule
```

1.9 WAVEFORM:

 

1.10 OBSERVATION:

In half subtractor, the difference of the two inputs is represented using logical XOR of A and Bin and borrow is represented using logical AND of logical NOT of A and Bin.


1.11 RESULT:

Half Subtractor is simulated and implemented in Data Flow Modeling.

2.1 AIM: To implement Full Subtractor

2.2 SOFTWARE USED: Xilinx Vivado 2022.2

2.3 SYMBOL:

 

2.4 LOGIC EXPRESSION:

$$D = A \oplus B \oplus Bin$$

$$Bout = (\sim(A) \& B) + (Bin \& (\sim(A \& B)))$$

2.5 BOOLEAN EXPRESSION:

$$D = \overline{A}(\overline{B}Cin + B\overline{Cin}) + A(\overline{B}Cin + B\overline{Cin})$$

$$Bout = \overline{A}B + Bin(AB + \overline{A}\overline{B})$$

2.6 TRUTH TABLE:

INPUT			OUTPUT	
A	B	Bin	D	Bout
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

2.7 VERILOG CODE (fullsubtractor_df.v):

```


module fullsubtractor_df(d,bout,a,b,bin);
    output d,bout;
    input a,b,bin;
    assign d = a^b^bin;
    assign bout = (~(a)&b)+(bin&(~(a^b)));
endmodule
    
```

2.8 TEST BENCH (fullsubtractor_df_tb.v):

```

module fullsubtractor_df_tb();
reg a,b,bin;
wire d,bout;
fullsubtractor_df x1(d,bout,a,b,bin);
initial
begin
    {a,b,bin}=3'b000;
    #10 {a,b,bin}=3'b001;
    #10 {a,b,bin}=3'b010;
    #10 {a,b,bin}=3'b011;
    #10 {a,b,bin}=3'b100;
    #10 {a,b,bin}=3'b101;
    #10 {a,b,bin}=3'b110;
    #10 {a,b,bin}=3'b111;
end
endmodule
    
```

2.9 WAVEFORM:

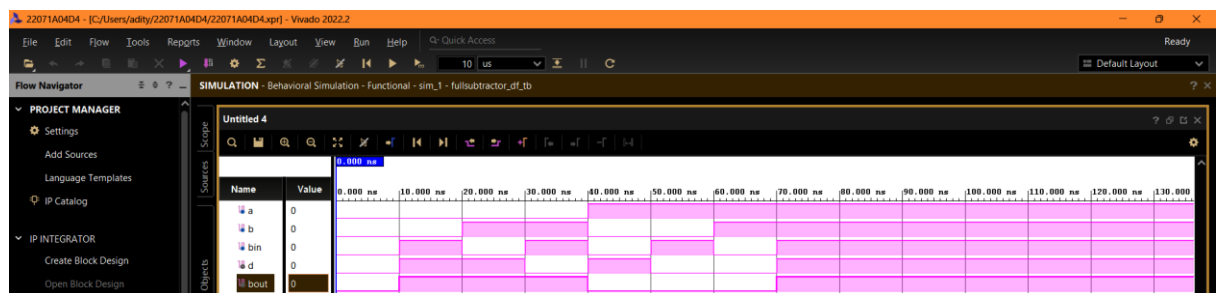


2.10 OBSERVATION:

In full subtractor, the sum of the two inputs is represented using $D = A \oplus B \oplus \text{Cin}$ and carry is represented using $\text{Bout} = (A \& B) + (B \& (A \oplus B))$

2.11 RESULT:

Full Subtractor is simulated and implemented in Data Flow Modeling.

 SUBTRACTORS (Behavioral Flow Modeling)**1.1 AIM:** To implement Half Subtractor**1.2 SOFTWARE USED:** Xilinx Vivado 2022.2**1.3 SYMBOL:****1.4 LOGIC EXPRESSION:**

$$D = A \oplus \text{Bin}$$

$$\text{Bout} = \sim(A) \& \text{Bin}$$

1.5 BOOLEAN EXPRESSION:

$$S = \bar{A}\text{Bin} + A\bar{\text{Bin}}$$

$$\text{Bout} = \bar{A}.B$$

1.6 TRUTH TABLE:

INPUT		OUTPUT	
A	Bin	D	Bout
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

1.7 VERILOG CODE (halfsubtractor_bf.v):

```

module halfsubtractor_bf(d,bout,a,bin);
    output d,bout;
    input a,bin;
    reg d,bout;
    always @(a,bin)
    begin
        if(a==1'b0 & bin==1'b0)
        begin
            d=0;


```

```
bout=0;
end
else if(a==1'b0 & bin==1'b1)
begin
d=1;
bout=1;
end
else if(a==1'b1 & bin==1'b0)
begin
d=1;
bout=0;
end
else if(a==1'b1 & bin==1'b1)
begin
d=0;
bout=0;
end
end
endmodule
```

1.8 TEST BENCH (halfsubtractor_df_tb.v):

```
module halfsubtractor_bf_tb();
reg a,bin;
wire d,bout;
halfsubtractor_bf x1(d,bout,a,bin);
initial
begin
{a,bin}=2'b00;
#10 {a,bin}=2'b01;
#20 {a,bin}=2'b10;
#40 {a,bin}=2'b11;
#60 $finish;
end
endmodule
```

1.9 WAVEFORM:

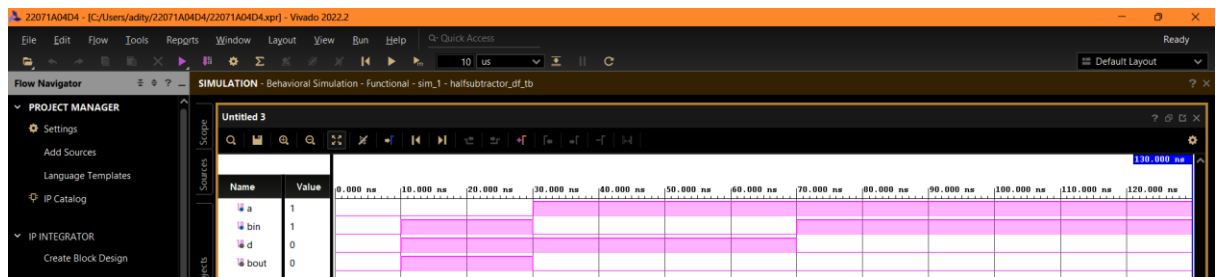

1.10 OBSERVATION:

In half subtractor, the difference of the two inputs is represented using logical XOR of A and Bin and borrow is represented using logical AND of logical NOT of A and Bin.


1.11 RESULT:

Half Subtractor is simulated and implemented in Behavioral Flow Modeling.

2.1 AIM: To implement Full Subtractor

2.2 SOFTWARE USED: Xilinx Vivado 2022.2

2.3 SYMBOL:

 

2.4 LOGIC EXPRESSION:

$$D = A \oplus B \oplus \text{Bin}$$

$$\text{Bout} = (\sim(A) \& B) + (\text{Bin} \& (\sim(A \& B)))$$

2.5 BOOLEAN EXPRESSION:

$$D = \overline{A}(\overline{B}\text{Cin} + B\text{Cin}) + A(\overline{B}\text{Cin} + B\text{Cin})$$

$$\text{Bout} = \overline{A}B + \text{Bin}(AB + \overline{A}B)$$

2.6 TRUTH TABLE:

INPUT			OUTPUT	
A	B	Bin	D	Bout
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

2.7 VERILOG CODE (fullsubtractor_bf.v):

```

module fullsubtractor_bf(d,bout,a,b,bin);
output d,bout;
input a,b,bin;
reg d,bout;
always@(a,b,bin)
begin
if(a==1'b0 & b==1'b0 & bin==1'b0)
begin
d=0;
bout = 0;
end
else if(a==1'b0 & b==1'b0 & bin==1'b1)
begin

```


```
d=1;
bout = 1;
end
else if(a==1'b0 & b==1'b1 & bin==1'b0)
begin
d=1;
bout = 1;
end
else if(a==1'b0 & b==1'b1 & bin==1'b1)
begin
d=0;
bout = 1;
end
else if(a==1'b1 & b==1'b0 & bin==1'b0)
begin
d=1;
bout = 0;
end
else if(a==1'b1 & b==1'b0 & bin==1'b1)
begin
d=0;
bout = 0;
end
else if(a==1'b1 & b==1'b1 & bin==1'b0)
begin
d=0;
bout = 0;
end
else if(a==1'b1 & b==1'b1 & bin==1'b1)
begin
d=1;
bout = 1;
end
else
begin
d=0;
bout = 0;
end
end
endmodule
```

2.8 TEST BENCH (fullsubtractor_bf_tb.v):

```

module fullsubtractor_bf_tb();
    reg a,b,bin;
    wire d,bout;
    fullsubtractor_bf x1(d,bout,a,b,bin);
    initial
    begin
        {a,b,bin}=3'b000;
        #10 {a,b,bin}=3'b001;
        #10 {a,b,bin}=3'b010;
        #10 {a,b,bin}=3'b011;
        #10 {a,b,bin}=3'b100;
        #10 {a,b,bin}=3'b101;
        #10 {a,b,bin}=3'b110;
        #10 {a,b,bin}=3'b111;
    end
end
endmodule
    
```

2.9 WAVEFORM:

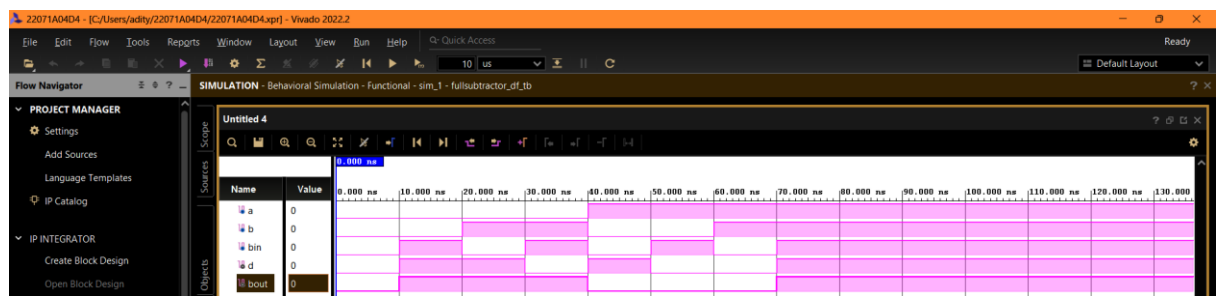


2.10 OBSERVATION:

In full subtractor, the sum of the two inputs is represented using $D = A \oplus B \oplus \text{Cin}$ and carry is represented using $\text{Bout} = (A \& B) + (\text{Bin} \& (A \oplus B))$

2.11 RESULT:

Full Subtractor is simulated and implemented in Behavioral Flow Modeling.

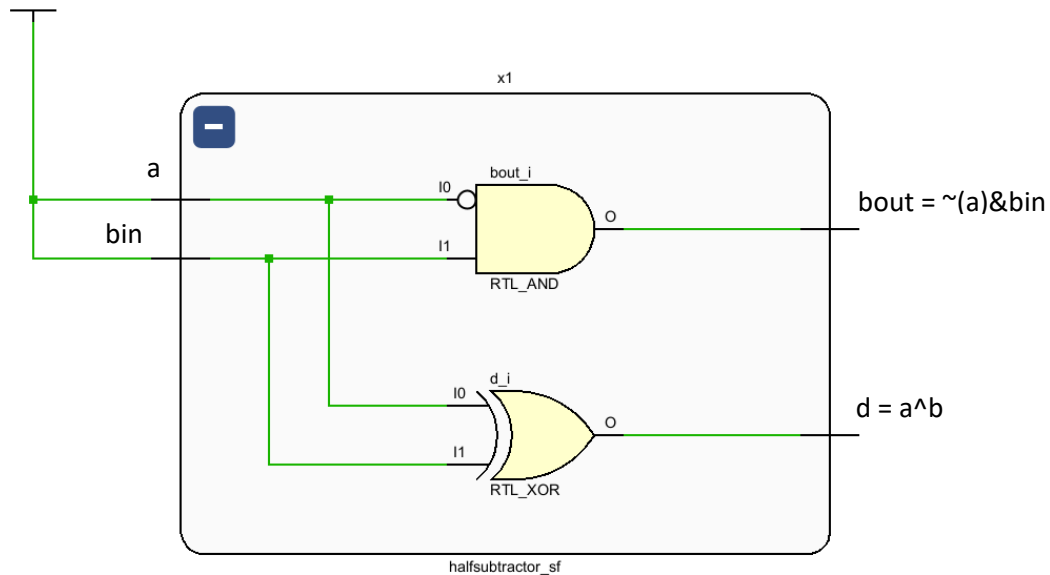SUBTRACTORS (Structural Flow Modeling)**1.1 AIM:** To implement Half Subtractor**1.2 SOFTWARE USED:** Xilinx Vivado 2022.2**1.3 SYMBOL:****1.4 LOGIC EXPRESSION:**

$$D = A \oplus \text{Bin}$$

$$\text{Bout} = \sim(A) \& \text{Bin}$$

1.5 BOOLEAN EXPRESSION:

$$S = \bar{A}\text{Bin} + A\bar{\text{Bin}}$$

$$\text{Bout} = \bar{A}.B$$

1.6 TRUTH TABLE:

INPUT		OUTPUT	
A	Bin	D	Bout
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

1.7 VERILOG CODE (halfsubtractor_sf.v):

```

module halfsubtractor_sf(d,bout,a,bin);
output d,bout;
input a,bin;
wire x;
xor (d,a,bin);
not (x,a);
and (bout,x,bin);
endmodule


```

1.8 TEST BENCH (halfsubtractor_sf_tb.v):

```

module halfsubtractor_sf_tb();
reg a,bin;
wire d,bout;
halfsubtractor_sf x1(d,bout,a,bin);
initial
begin
{a,bin}=2'b00;
#10 {a,bin}=2'b01;
#20 {a,bin}=2'b10;
#40 {a,bin}=2'b11;
#60 $finish;
end
endmodule
    
```

1.9 WAVEFORM:

 

1.10 OBSERVATION:

In half subtractor, the difference of the two inputs is represented using logical XOR of A and Bin and borrow is represented using logical AND of logical NOT of A and Bin.


1.11 RESULT:

Half Subtractor is simulated and implemented in Structural Flow Modeling.

2.1 AIM: To implement Full Subtractor

2.2 SOFTWARE USED: Xilinx Vivado 2022.2

2.3 SYMBOL:

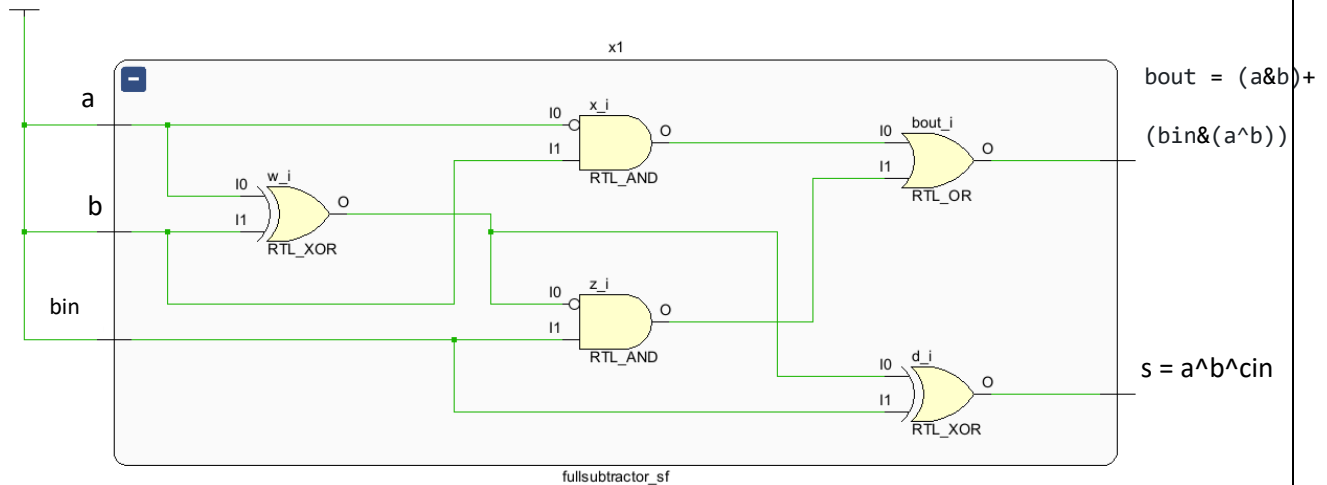

2.4 LOGIC EXPRESSION:

$$D = A \oplus B \oplus \text{Bin}$$

$$\text{Bout} = (\sim(A) \& B) + (\text{Bin} \& (\sim(A \& B)))$$

2.5 BOOLEAN EXPRESSION:

$$D = \overline{A}(\overline{B}\text{Cin} + B\overline{\text{Cin}}) + A(\overline{B}\text{Cin} + B\overline{\text{Cin}})$$

$$\text{Bout} = \overline{A}B + \text{Bin}(AB + \overline{A}\overline{B})$$

2.6 TRUTH TABLE:

INPUT			OUTPUT	
A	B	Bin	D	Bout
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

2.7 VERILOG CODE (fullsubtractor_sf.v):

```

module fullsubtractor_sf (d,bout,a,b,bin);
    output d,bout;
    input a,b,bin;
    wire w,x,y,z;
    xor (w,a,b);
    xor (d,w,bin);
    and (x,~a,b);


```

```
xnor (y,a,b);
and (z,y,bin);
or (bout,x,z);
endmodule
```

2.8 TEST BENCH (fullsubtractor_sf_tb.v):

```
module fullsubtractor_sf_tb();
reg a,b,bin;
wire d,bout;
fullsubtractor_sf x1(d,bout,a,b,bin);
initial
begin
{a,b,bin}=3'b000;
#10 {a,b,bin}=3'b001;
#10 {a,b,bin}=3'b010;
#10 {a,b,bin}=3'b011;
#10 {a,b,bin}=3'b100;
#10 {a,b,bin}=3'b101;
#10 {a,b,bin}=3'b110;
#10 {a,b,bin}=3'b111;
end
endmodule
```

2.9 WAVEFORM:

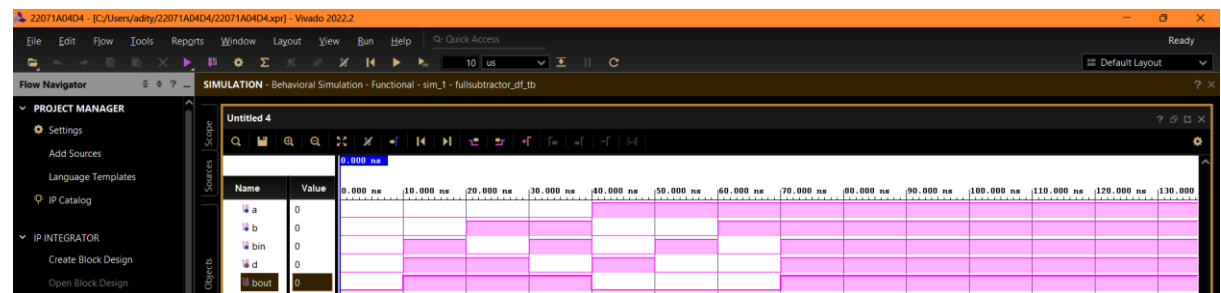

2.10 OBSERVATION:

In full subtractor, the sum of the two inputs is represented using $D = A \oplus B \oplus C_{in}$ and carry is represented using $Bout = (A \& B) + (Bin \& (A \oplus B))$

2.11 RESULT:

Full Subtractor is simulated and implemented in Structural Flow Modeling.