

**LIST OF EXPERIMENTS**

Cycle I:

Part-1

To Verify the Functionality of the following 74 Series ICs:

1. 3- 8 Decoder – 74LS138.
2. 8X1 Multiplexer– 74151 and 2X4 De-multiplexer- 74155.
3. 2-bit COMPARATOR -74LS85.
4. D-Flip- Flop – (74LS74) and JK Flip- Flop (74LS73).

Part-2

Design and simulate the following Circuits using HDL:

1. Logic Gates.
2. Adders and Subtractors
3. Code converters
4. Multiplexer and De-multiplexer.
5. Encoder and Decoder.
6. Parity generator and checker
7. Flip Flops using Truth table and FSM
8. Shift Registers
9. Asynchronous counters
10. Synchronous counters

Cycle II:

1. Development of one application which shall cover maximum no. of Experiments in Cycle I.

**EXPERIMENT-1**

**REALIZATION OF LOGIC GATES (NOT, AND, OR, NAND, NOR, XOR, XNOR)**


1. **AIM:** To Design, simulate and implement all Logic Gates in 3 different modeling styles(Data Flow, Behavioral Flow, Structural Flow Modeling)
2. **SOFTWARE USED:** Xilinx Vivado 2022.2
3. **PROCEDURE:**
  - Open the Xilinx Vivado project navigator.
  - Open the Design source and go to add / create sources
  - Create new file, give appropriate name save it.
  - Open the file in the editor and write the Verilog code.
  - Open the Design source and go to add / create sources to create the test bench
  - Open the editor and write the Verilog code for test bench.
  - After completion of Verilog code set your test bench as top module in simulation settings and Run Simulation.
  - To view RTL schematic, select RTL Analysis in which select open elaborate design, select Schematic.

## LOGIC GATES (Data Flow Modeling)

**1.1 AIM:** To implement AND Gate

**1.2 SOFTWARE USED:** Xilinx Vivado 2022.2

**1.3 SYMBOL:**

 

**1.4 LOGIC EXPRESSION:**

$$Y = (A \& B)$$

**1.5 BOOLEAN EXPRESSION:**

$$Y = (A.B)$$

**1.6 TRUTH TABLE:**

INPUT		OUTPUT
A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

**1.7 VERILOG CODE (andgate\_df.v):**

```

module andgate_df(y,a,b);
    output y;
    input a,b;


    assign y=a&b;

endmodule
    
```

### 1.8 TEST BENCH CODE (andgate\_df\_tb.v):

```
module andgate_tb();  
    reg a,b;  
    wire y;  
    andgate_df x1(y,a,b);  
    initial  
    begin  
        a=1'b0; b=1'b0;  
        #10 a=1'b0; b=1'b1;  
        #20 a=1'b1; b=1'b0;  
        #40 a=1'b1; b=1'b1;  
        #60 $finish;  
    end  
endmodule
```

### 1.9 WAVEFORM:

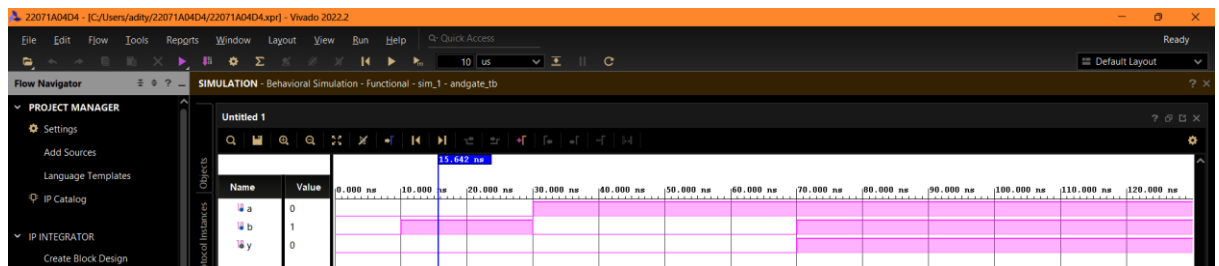

### 1.10 OBSERVATION:

Output is high for both high inputs and low for all other cases.


### 1.11 RESULT:

The Logical AND Gate is simulated and implemented in Data Flow Modeling.

**2.1 AIM:** To implement OR Gate

**2.2 SOFTWARE USED:** Xilinx Vivado 2022.2

**2.3 SYMBOL:**

 

**2.4 LOGIC EXPRESSION:**

$$Y = (A|B)$$

**2.5 BOOLEAN EXPRESSION:**

$$Y = (A+B)$$

**2.6 TRUTH TABLE:**

INPUT		OUTPUT
A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

**2.7 VERILOG CODE (orgate\_df.v):**


```
module orgate_df(y,a,b);  
    output y;  
    input a,b;  
  
    assign y=a|b;
```

```
endmodule
```

### 2.8 TEST BENCH CODE (orgate\_df\_tb.v):

```
module orgate_tb();  
    reg a,b;  
    wire y;  
    orgate_df x1(y,a,b);  
    initial  
    begin  
        a=1'b0; b=1'b0;  
        #10 a=1'b0; b=1'b1;  
        #20 a=1'b1; b=1'b0;  
        #40 a=1'b1; b=1'b1;  
        #60 $finish;  
    end  
endmodule
```

### 2.9 WAVEFORM:

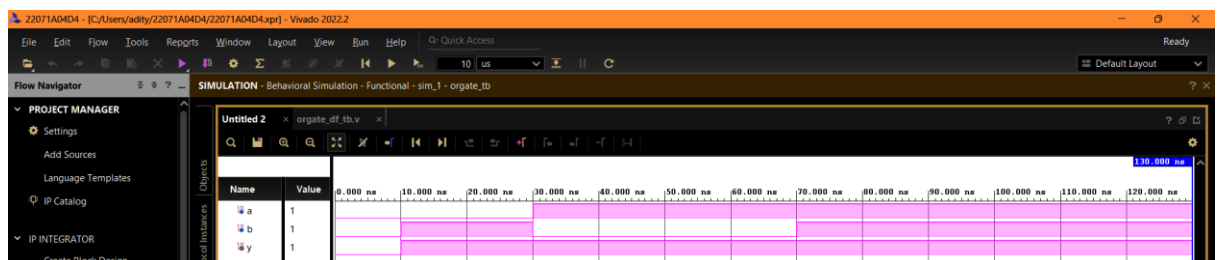

### 2.10 OBSERVATION:

Output is low for both low inputs and high for all other cases.


### 2.11 RESULT:

The Logical OR Gate is simulated and implemented in Data Flow Modeling.

**3.1 AIM:** To implement NAND Gate

**3.2 SOFTWARE USED:** Xilinx Vivado 2022.2

**3.3 SYMBOL:**

 

**3.4 LOGICAL EXPRESSION:**

$$Y = \sim(A \& B)$$

**3.5 BOOLEAN EXPRESSION:**

$$Y = \overline{(A \cdot B)}$$

**3.6 TRUTH TABLE:**

INPUT		OUTPUT
A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

**3.7 VERILOG CODE (nandgate\_df.v):**

```

module nandgate_df(y,a,b);
    output y;
    input a,b;


    assign y=~(a&b);

endmodule
    
```

### 3.8 TEST BENCH CODE (nandgate\_df\_tb.v):

```
module nandgate_tb();  
    reg a,b;  
    wire y;  
    nandgate_df x1(y,a,b);  
    initial  
    begin  
        a=1'b0; b=1'b0;  
        #10 a=1'b0; b=1'b1;  
        #20 a=1'b1; b=1'b0;  
        #40 a=1'b1; b=1'b1;  
        #60 $finish;  
    end  
endmodule
```

### 3.9 WAVEFORM:

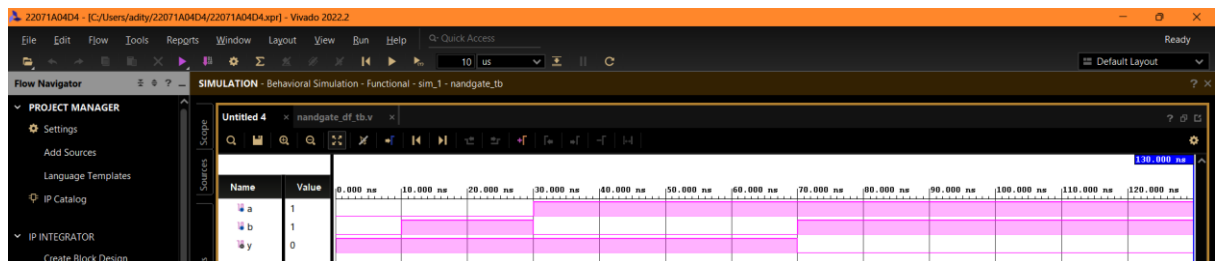

### 3.10 OBSERVATION:

Output is low for both high inputs and high for all other cases.

### 3.11 RESULT:


The Logical NAND Gate is simulated and implemented in Data Flow Modeling.



**4.1 AIM:** To implement NOR Gate

**4.2 SOFTWARE USED:** Xilinx Vivado 2022.2

**4.3 SYMBOL:**

 

**4.4 LOGICAL EXPRESSION:**

$$Y = \sim(A|B)$$

**4.5 BOOLEAN EXPRESSION:**

$$Y = \overline{(A+B)}$$

**4.6 TRUTH TABLE:**

INPUT		OUTPUT
A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

**4.7 VERILOG CODE (norgate\_df.v):**

```

module norgate_df(y,a,b);
    output y;
    input a,b;


    assign y=~(a|b);

endmodule
    
```

### 4.8 TEST BENCH CODE (norgate\_df\_tb.v):

```
module norgate_tb();  
    reg a,b;  
    wire y;  
    norgate_df x1(y,a,b);  
    initial  
    begin  
        a=1'b0; b=1'b0;  
        #10 a=1'b0; b=1'b1;  
        #20 a=1'b1; b=1'b0;  
        #40 a=1'b1; b=1'b1;  
        #60 $finish;  
    end  
endmodule
```

### 4.9 WAVEFORM:

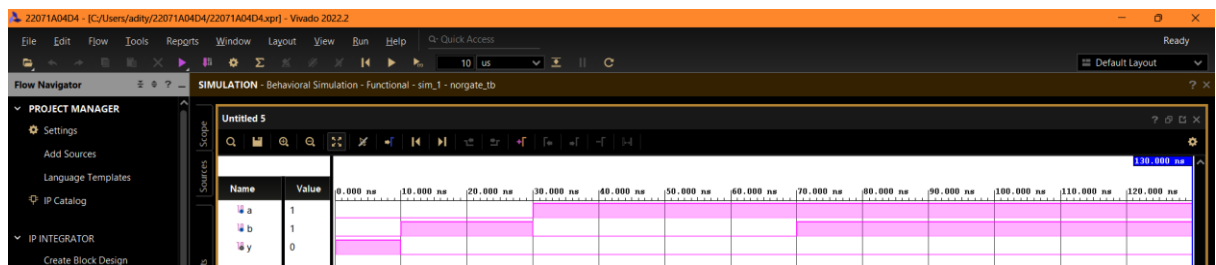

### 4.10 OBSERVATION:

Output is high for both low inputs and low for all other cases.


### 4.11 RESULT:

The Logical NOR Gate is simulated and implemented in Data Flow Modeling.

**5.1 AIM:** To implement NOT Gate

**5.2 SOFTWARE USED:** Xilinx Vivado 2022.2

**5.3 SYMBOL:**

 

**5.4 LOGICAL EXPRESSION:**

$$Y = \sim(A)$$

**5.5 BOOLEAN EXPRESSION:**

$$Y = \overline{A}$$

**5.6 TRUTH TABLE:**

INPUT	OUTPUT
A	Y
0	1
1	0


**5.7 VERILOG CODE (notgate\_df.v):**

```
module notgate_df(y,a);  
    output y;  
    input a;  
  
    assign y=~(a);  
  
endmodule
```

### 5.8 TEST BENCH CODE (notgate\_df\_tb.v):

```
module notgate_tb();  
    reg a;  
    wire y;  
    notgate_df x1(y,a);  
    initial  
    begin  
        a=1'b0; b=1'b0;  
        #10 a=1'b0; b=1'b1;  
        #10 $finish;  
    end  
endmodule
```

### 5.9 WAVEFORM:

 

### 5.10 OBSERVATION:

Output is high for low input and low for high input.


### 5.11 RESULT:

The Logical NOT Gate is simulated and implemented in Data Flow Modeling.

**6.1 AIM:** To implement XOR Gate

**6.2 SOFTWARE USED:** Xilinx Vivado 2022.2

**6.3 SYMBOL:**

 

**6.4 LOGICAL EXPRESSION:**

$$Y = A \oplus B$$

**6.5 BOOLEAN EXPRESSION:**

$$Y = (\overline{A}B + A\overline{B})$$

**6.6 TRUTH TABLE:**

INPUT		OUTPUT
A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

**6.7 VERILOG CODE (xorgate\_df.v):**

```

module xorgate_df(y,a,b);
    output y;
    input a,b;


    assign y=(a^b);

endmodule
    
```

### 6.8 TEST BENCH CODE (xorgate\_df\_tb.v):

```
module xorgate_tb();
    reg a,b;
    wire y;
    xorgate_df x1(y,a,b);
    initial
    begin
        a=1'b0; b=1'b0;
        #10 a=1'b0; b=1'b1;
        #20 a=1'b1; b=1'b0;
        #40 a=1'b1; b=1'b1;
        #60 $finish;
    end
endmodule
```

### 6.9 WAVEFORM:

 

### 6.10 OBSERVATION:

Output is low for both same inputs and high for all other cases.


### 6.11 RESULT:

The Logical XOR Gate is simulated and implemented in Data Flow Modeling.

**7.1 AIM:** To implement XNOR Gate

**7.2 SOFTWARE USED:** Xilinx Vivado 2022.2

**7.3 SYMBOL:**

 

**7.4 LOGICAL EXPRESSION:**

$$Y = \sim(A \wedge B)$$

**7.5 BOOLEAN EXPRESSION:**

$$Y = (A.B + \overline{A.B})$$

**7.6 TRUTH TABLE:**

INPUT		OUTPUT
A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

**7.7 VERILOG CODE (xnorgate\_df.v):**

```

module xnorgate_df(y,a,b);
    output y;
    input a,b;

    assign y=~(a^b);


endmodule
    
```

### 7.8 TEST BENCH CODE (xnorgate\_df\_tb.v):

```

module xnorgate_tb();
    reg a,b;
    wire y;
    xnorgate_df x1(y,a,b);
    initial
    begin
        a=1'b0; b=1'b0;
        #10 a=1'b0; b=1'b1;
        #20 a=1'b1; b=1'b0;
        #40 a=1'b1; b=1'b1;
        #60 $finish;
    end
endmodule
    
```

### 7.9 WAVEFORM:

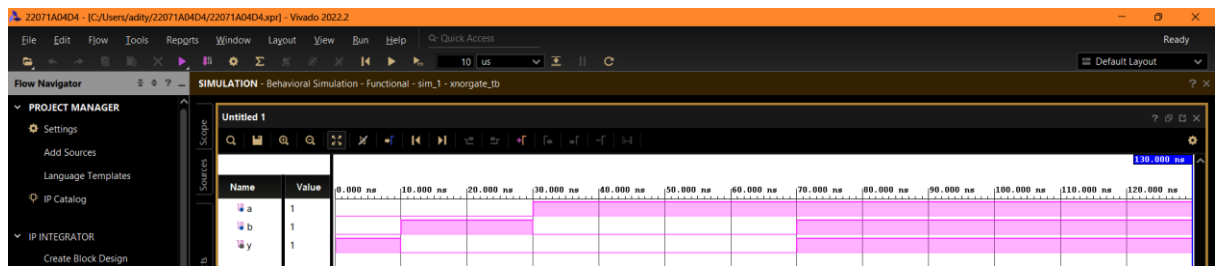

### 7.10 OBSERVATION:

Output is high for both same inputs and low for all other cases.

### 7.11 RESULT:

The Logical XNOR Gate is simulated and implemented in Data Flow Modeling.




## LOGIC GATES (Behavioral Flow Modeling)

**1.12 AIM:** To implement AND Gate

**1.13 SOFTWARE USED:** Xilinx Vivado 2022.2

**1.14 SYMBOL:**

 

**1.15 LOGICAL EXPRESSION:**

$$Y = (A \& B)$$

**1.16 BOOLEAN EXPRESSION:**

$$Y = (A.B)$$

**1.17 TRUTH TABLE:**

INPUT		OUTPUT
A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

**1.18 VERILOG CODE (andgate\_bf.v):**

```
module andgate_bf(y,a,b);
    output y;
    input a,b;
    reg y;
    always@(a,b)
    begin
        if(a==1'b1 & b==1'b1)
```

```

y=1;
else
y=0;
end
endmodule

```


### 1.19 TEST BENCH CODE (andgate\_bf\_tb.v):

```

module andgate_bf_tb();
reg a,b;
wire y;
andgate_bf x1(y,a,b);
initial
begin
    a=1'b0; b=1'b0;
    #10 a=1'b0; b=1'b1;
    #20 a=1'b1; b=1'b0;
    #40 a=1'b1; b=1'b1;
    #60 $finish;
end
endmodule

```

### 1.20 WAVEFORM:

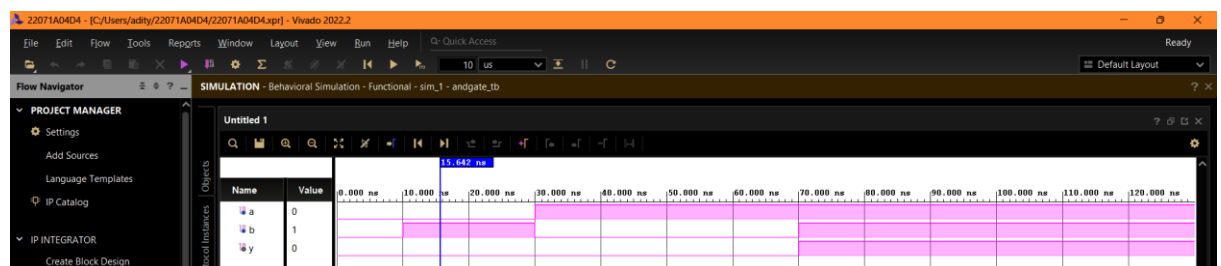

### 1.21 OBSERVATION:

Output is high for both high inputs and low for all other cases.


### 1.22 RESULT:

The Logical AND Gate is simulated and implemented in Behavioral Flow Modeling.

**2.1 AIM:** To implement OR Gate

**2.2 SOFTWARE USED:** Xilinx Vivado 2022.2

**2.3 SYMBOL:**

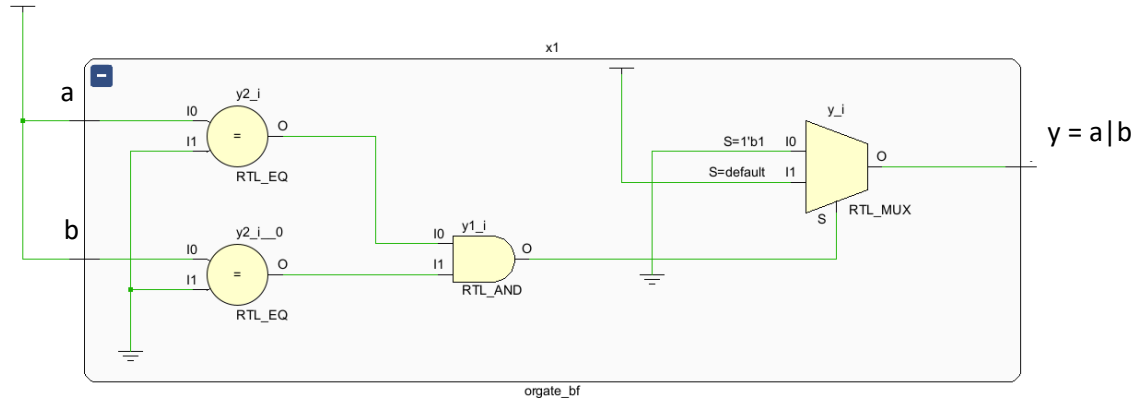

**2.4 LOGICAL EXPRESSION:**

$$Y = A|B$$

**2.5 BOOLEAN EXPRESSION:**

$$Y = (A+B)$$

**2.6 TRUTH TABLE:**

INPUT		OUTPUT
A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

**2.7 VERILOG CODE (orgate\_bf.v):**


```

module orgate_bf(y,a,b);
    output y;
    input a,b;
    reg y;
    always@(a,b)
    begin
        if(a==1'b0 & b==1'b0)
            y=0;
        else
            y=1;
        end
    endmodule
    
```

### 2.8 TEST BENCH CODE (orgate\_bf\_tb.v):

```
module orgate_bf_tb();  
    reg a,b;  
    wire y;  
    orgate_bf x1(y,a,b);  
    initial  
    begin  
        a=1'b0; b=1'b0;  
        #10 a=1'b0; b=1'b1;  
        #20 a=1'b1; b=1'b0;  
        #40 a=1'b1; b=1'b1;  
        #60 $finish;  
    end  
endmodule
```

### 2.9 WAVEFORM:

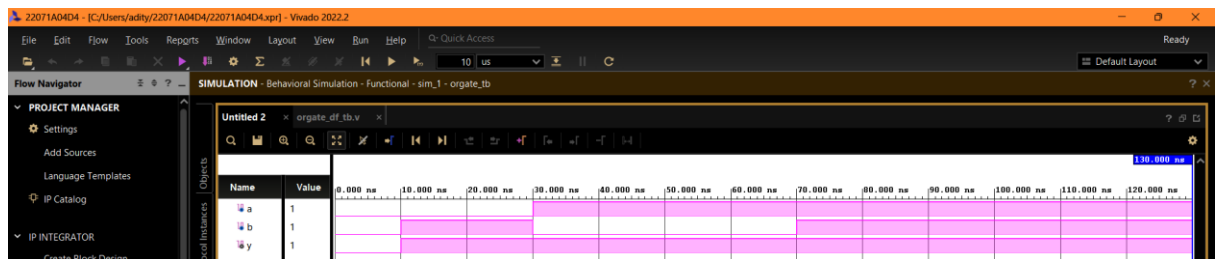

### 2.10 OBSERVATION:

Output is low for both low inputs and high for all other cases.


### 2.11 RESULT:

The Logical OR Gate is simulated and implemented in Behavioral Flow Modeling.

**3.1 AIM:** To implement NAND Gate

**3.2 SOFTWARE USED:** Xilinx Vivado 2022.2

**3.3 SYMBOL:**

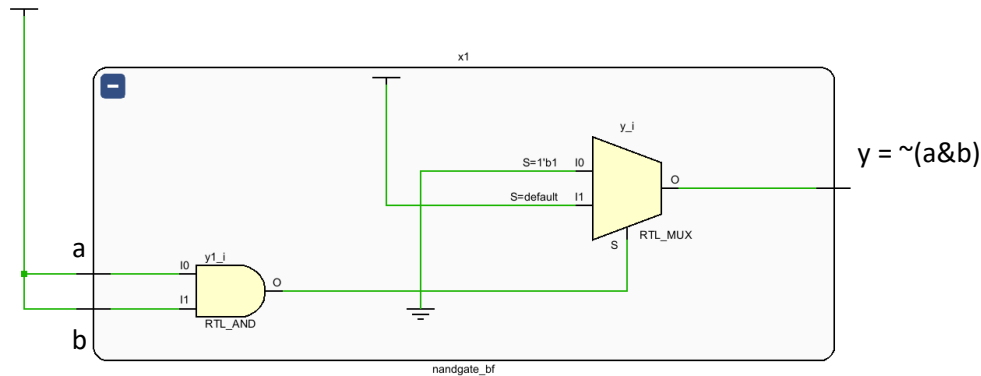

**3.4 LOGICAL EXPRESSION:**

$$Y = \sim(A \& B)$$

**3.5 BOOLEAN EXPRESSION:**

$$Y = \overline{(A \cdot B)}$$

**3.6 TRUTH TABLE:**

INPUT		OUTPUT
A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

**3.7 VERILOG CODE (nandgate\_bf.v):**

```

module nandgate_bf(y,a,b);
output y;
input a,b;
reg y;
always@(a,b)
begin
if(a==1'b1 & b==1'b1)


```

```
y=0;  
else  
y=1;  
end  
endmodule
```

### 3.8 TEST BENCH CODE (nandgate\_bf\_tb.v):

```
module nandgate_bf_tb();  
    reg a,b;  
    wire y;  
    nandgate_bf x1(y,a,b);  
    initial  
    begin  
        a=1'b0; b=1'b0;  
        #10 a=1'b0; b=1'b1;  
        #20 a=1'b1; b=1'b0;  
        #40 a=1'b1; b=1'b1;  
        #60 $finish;  
    end  
endmodule
```

### 3.9 WAVEFORM:

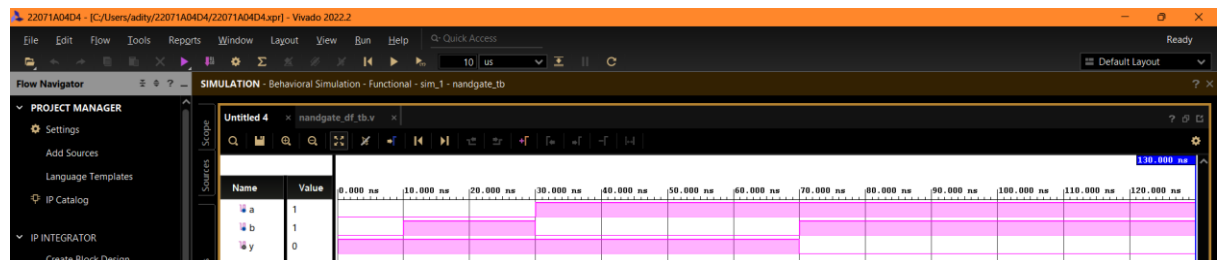

### 3.10 OBSERVATION:

Output is low for both high inputs and high for all other cases.


### 3.11 RESULT:

The Logical NAND Gate is simulated and implemented in Behavioral Flow Modeling.

**4.1 AIM:** To implement NOR Gate

**4.2 SOFTWARE USED:** Xilinx Vivado 2022.2

**4.3 SYMBOL:**

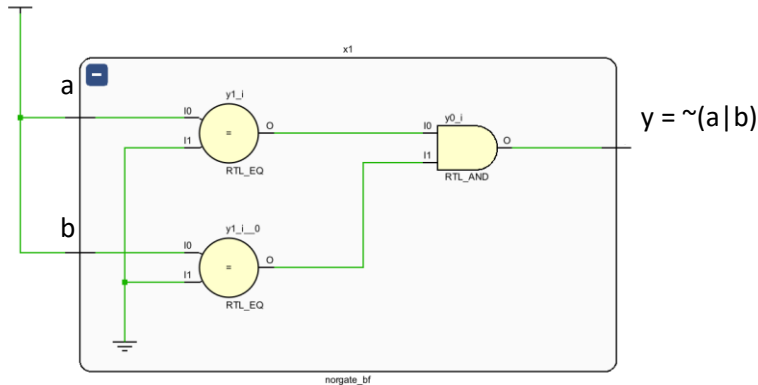

**4.4 LOGICAL EXPRESSION:**

$$Y = \sim(A|B)$$

**4.5 BOOLEAN EXPRESSION:**

$$Y = \overline{(A+B)}$$

**4.6 TRUTH TABLE:**

INPUT		OUTPUT
A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

**4.7 VERILOG CODE (norgate\_bf.v):**

```

module norgate_bf(y,a,b);
output y;
input a,b;
reg y;
always@(a,b)
begin
if(a==1'b0 & b==1'b0)
y=1;
else
y=0;
end


```

```
endmodule
```

#### 4.8 TEST BENCH CODE (norgate\_bf\_tb.v):

```
module norgate_bf_tb();
    reg a,b;
    wire y;
    norgate_bf x1(y,a,b);
    initial
    begin
        a=1'b0; b=1'b0;
        #10 a=1'b0; b=1'b1;
        #20 a=1'b1; b=1'b0;
        #40 a=1'b1; b=1'b1;
        #60 $finish;
    end
endmodule
```

#### 4.9 WAVEFORM:

 

#### 4.10 OBSERVATION:

Output is high for both low inputs and low for all other cases.

#### 4.11 RESULT:


The Logical NOR Gate is simulated and implemented in Behavioral Flow Modeling.



**5.1 AIM:** To implement NOT Gate

**5.2 SOFTWARE USED:** Xilinx Vivado 2022.2

**5.3 SYMBOL:**

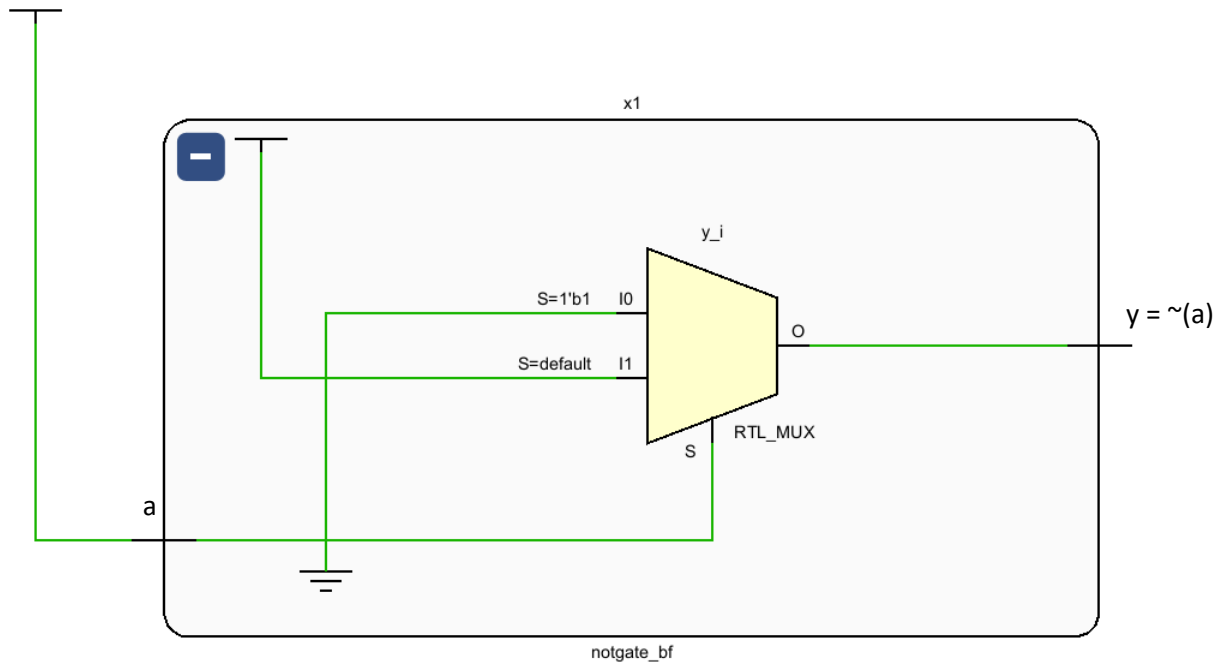

**5.4 LOGIC EXPRESSION:**

$$Y = \sim(A)$$

**5.5 BOOLEAN EXPRESSION:**

$$Y = \overline{A}$$

**5.6 TRUTH TABLE:**

INPUT	OUTPUT
A	Y
0	1
1	0

**5.7 VERILOG CODE (notgate\_bf.v):**

```

module notgate_bf(y,a);
    output y;
    input a;
    reg y;
    always@(a)


```

```
begin
if(a==1'b1)
y=0;
else
y=1;
end
endmodule
```

### 5.8 TEST BENCH CODE (notgate\_bf\_tb.v):

```
module notgate_bf_tb();
reg a;
wire y;
notgate_bf x1(y,a);
initial
begin
a=1'b0; b=1'b0;
#10 a=1'b0; b=1'b1;
#10 $finish;
end
endmodule
```

### 5.9 WAVEFORM:

 

### 5.10 OBSERVATION:

Output is high for low input and low for high input.


### 5.11 RESULT:

The Logical NOT Gate is simulated and implemented in Behavioral Flow Modeling.

**6.1 AIM:** To implement XOR Gate

**6.2 SOFTWARE USED:** Xilinx Vivado 2022.2

**6.3 SYMBOL:**

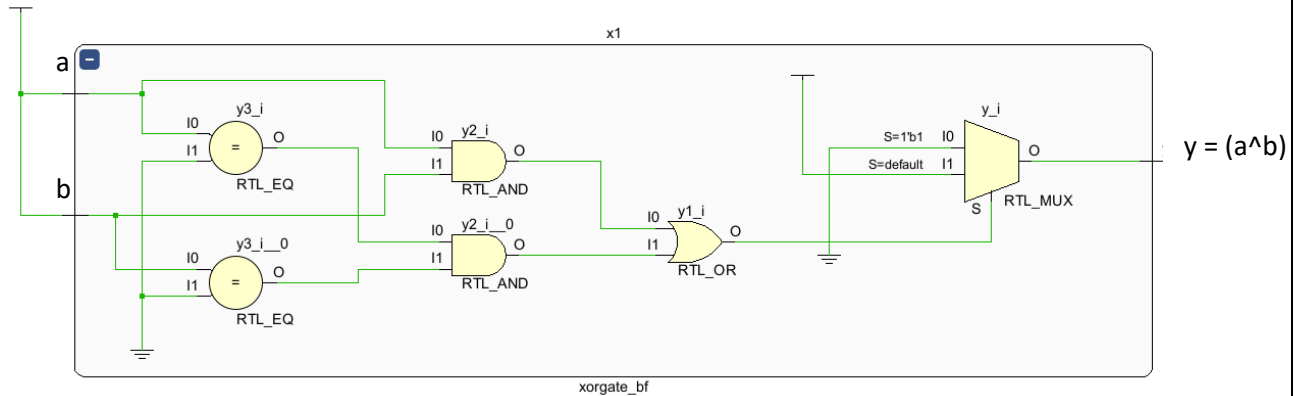

**6.4 LOGIC EXPRESSION:**

$$Y = A \oplus B$$

**6.5 BOOLEAN EXPRESSION:**

$$Y = (\bar{A}B + A\bar{B})$$

**6.6 TRUTH TABLE:**

INPUT		OUTPUT
A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

**6.7 VERILOG CODE (xorgate\_bf.v):**


```

module xorgate_bf(y,a,b);
output y;
input a,b;
reg y;
always@(a,b)
begin
if((a==1'b1 & b==1'b1)|(a==1'b0 & b==1'b0))
y=0;
else
y=1;
end
endmodule
    
```

### 6.8 TEST BENCH CODE (xorgate\_bf\_tb.v):

```
module xorgate_bf_tb();  
    reg a,b;  
    wire y;  
    xorgate_bf x1(y,a,b);  
    initial  
    begin  
        a=1'b0; b=1'b0;  
        #10 a=1'b0; b=1'b1;  
        #20 a=1'b1; b=1'b0;  
        #40 a=1'b1; b=1'b1;  
        #60 $finish;  
    end  
endmodule
```

### 6.9 WAVEFORM:

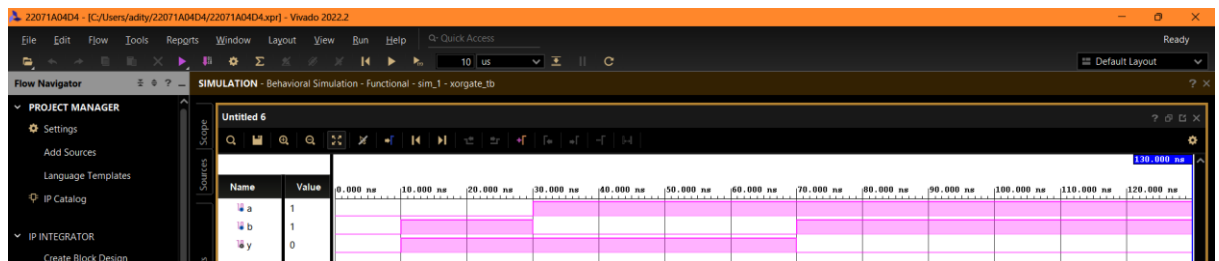

### 6.10 OBSERVATION:

Output is low for both same inputs and high for all other cases.


### 6.11 RESULT:

The Logical XOR Gate is simulated and implemented in Behavioral Flow Modeling.

**7.1 AIM:** To implement XNOR Gate

**7.2 SOFTWARE USED:** Xilinx Vivado 2022.2

**7.3 SYMBOL:**

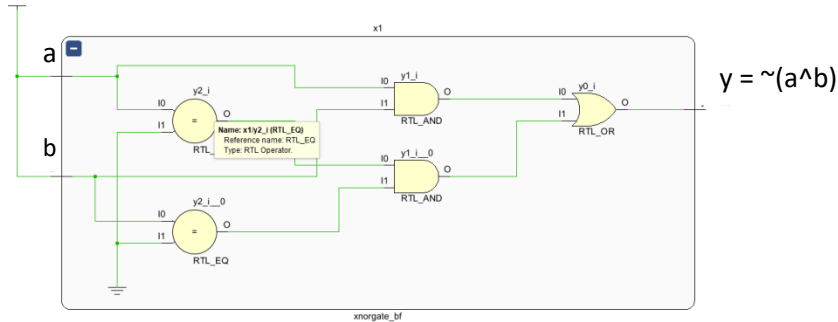

**7.4 LOGIC EXPRESSION:**

$$Y = \sim(A \wedge B)$$

**7.5 BOOLEAN EXPRESSION:**

$$Y = (A.B + \overline{A.B})$$

**7.6 TRUTH TABLE:**

INPUT		OUTPUT
A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

**7.7 VERILOG CODE (xnorgate\_bf.v):**


```

module xnorgate_bf(y,a,b);
    output y;
    input a,b;
    reg y;
    always@(a,b)
    begin
        if((a==1'b1 & b==1'b1)|(a==1'b0 & b==1'b0))
            y=1;
        else
            y=0;
        end
    endmodule
    
```

### 7.8 TEST BENCH CODE (xnorgate\_bf\_tb.v):

```
module xnorgate_bf_tb();  
    reg a,b;  
    wire y;  
    xnorgate_bf x1(y,a,b);  
    initial  
    begin  
        a=1'b0; b=1'b0;  
        #10 a=1'b0; b=1'b1;  
        #20 a=1'b1; b=1'b0;  
        #40 a=1'b1; b=1'b1;  
        #60 $finish;  
    end  
endmodule
```

### 7.9 WAVEFORM:

 

### 7.10 OBSERVATION:

Output is high for both same inputs and low for all other cases.

### 7.11 RESULT:


The Logical XNOR Gate is simulated and implemented in Behavioral Flow Modeling.

## LOGIC GATES (Structural Flow Modeling)

**1.1 AIM:** To implement AND Gate

**1.2 SOFTWARE USED:** Xilinx Vivado 2022.2

**1.3 SYMBOL:**

 

**1.4 LOGIC EXPRESSION:**

$$Y = (A \& B)$$

**1.5 BOOLEAN EXPRESSION:**

$$Y = (A.B)$$

**1.6 TRUTH TABLE:**

INPUT		OUTPUT
A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

**1.7 VERILOG CODE (andgate\_sf.v):**

```


module andgate_sf(y,a,b);
    output y;
    input a,b;
    wire y;
    and (y,a,b);
endmodule

```

### 1.8 TEST BENCH CODE (andgate\_sf\_tb.v):

```
module andgate_sf_tb();  
    reg a,b;  
    wire y;  
    andgate_sf x1(y,a,b);  
    initial  
    begin  
        a=1'b0; b=1'b0;  
        #10 a=1'b0; b=1'b1;  
        #20 a=1'b1; b=1'b0;  
        #40 a=1'b1; b=1'b1;  
        #60 $finish;  
    end  
endmodule
```

### 1.9 WAVEFORM:

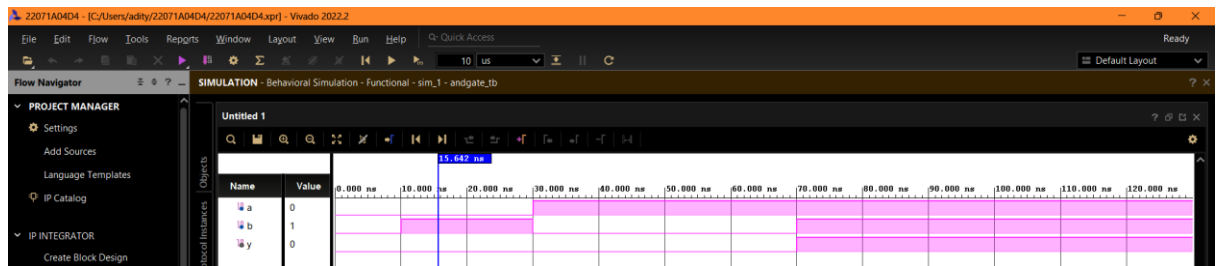

### 1.10 OBSERVATION:

Output is high for both high inputs and low for all other cases.

### 1.11 RESULT:


The Logical AND Gate is simulated and implemented in Structural Flow Modeling.



**2.1 AIM:** To implement OR Gate

**2.2 SOFTWARE USED:** Xilinx Vivado 2022.2

**2.3 SYMBOL:**

 

**2.4 LOGIC EXPRESSION:**

$$Y = (A|B)$$

**2.5 BOOLEAN EXPRESSION:**

$$Y = (A+B)$$

**2.6 TRUTH TABLE:**

INPUT		OUTPUT
A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

**2.7 VERILOG CODE (orgate\_sf.v):**

```

module orgate_sf(y,a,b);
    output y;
    input a,b;
    wire y;
    or (y,a,b);
endmodule

```

**2.8 TEST BENCH CODE (orgate\_sf\_tb.v):**


```

module orgate_sf_tb();
    reg a,b;
    wire y;

```

```
orgate_sf x1(y,a,b);  
initial  
begin  
    a=1'b0; b=1'b0;  
    #10 a=1'b0; b=1'b1;  
    #20 a=1'b1; b=1'b0;  
    #40 a=1'b1; b=1'b1;  
    #60 $finish;  
end  
endmodule
```

### 2.9 WAVEFORM:

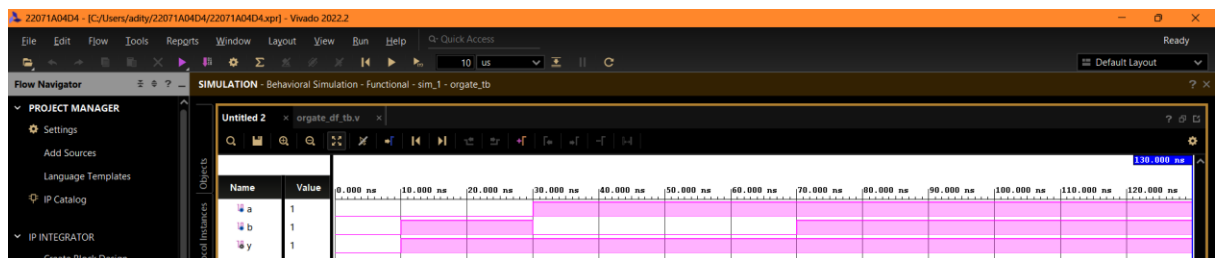

### 2.10 OBSERVATION:

Output is low for both low inputs and high for all other cases.


### 2.11 RESULT:

The Logical OR Gate is simulated and implemented in Structural Flow Modeling.

**3.1 AIM:** To implement NAND Gate

**3.2 SOFTWARE USED:** Xilinx Vivado 2022.2

**3.3 SYMBOL:**

 

**3.4 LOGIC EXPRESSION:**

$$Y = \sim(A \& B)$$

**3.5 BOOLEAN EXPRESSION:**

$$Y = \overline{(A \cdot B)}$$

**3.6 TRUTH TABLE:**

INPUT		OUTPUT
A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

**3.7 VERILOG CODE (nandgate\_sf.v):**


```
module nandgate_sf(y,a,b);
    output y;
    input a,b;
    wire y;
    nand (y,a,b);
endmodule
```

**3.8 TEST BENCH CODE (nandgate\_sf\_tb.v):**

```
module nandgate_sf_tb();
    reg a,b;
    wire y;
    nandgate_sf x1(y,a,b);
    initial
    begin
```

```
a=1'b0; b=1'b0;  
#10 a=1'b0; b=1'b1;  
#20 a=1'b1; b=1'b0;  
#40 a=1'b1; b=1'b1;  
#60 $finish;  
end  
endmodule
```

### 3.9 WAVEFORM:

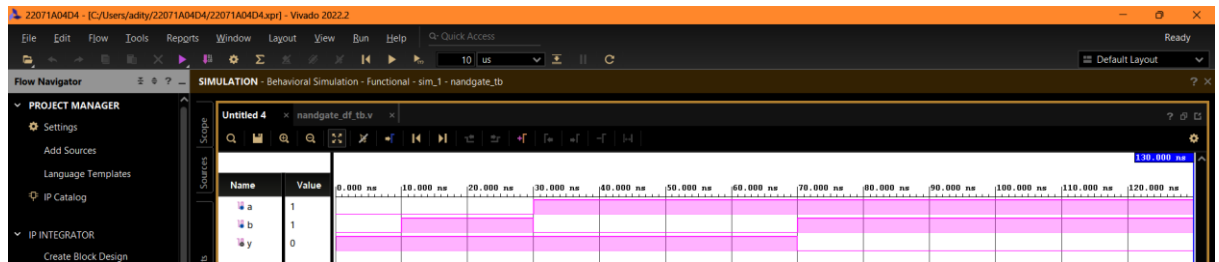

### 3.10 OBSERVATION:

Output is low for both high inputs and high for all other cases.


### 3.11 RESULT:

The Logical NAND Gate is simulated and implemented in Structural Flow Modeling.

**4.1 AIM:** To implement NOR Gate

**4.2 SOFTWARE USED:** Xilinx Vivado 2022.2

**4.3 SYMBOL:**

 

**4.4 LOGIC EXPRESSION:**

$$Y = \sim(A|B)$$

**4.5 BOOLEAN EXPRESSION:**

$$Y = \overline{(A+B)}$$

**4.6 TRUTH TABLE:**

INPUT		OUTPUT
A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

**4.7 VERILOG CODE (norgate\_sf.v):**


```
module norgate_sf(y,a,b);
    output y;
    input a,b;
    wire y;
    nor (y,a,b);
endmodule
```

**4.8 TEST BENCH CODE (norgate\_sf\_tb.v):**

```
module norgate_sf_tb();
    reg a,b;
    wire y;
    norgate_sf x1(y,a,b);
    initial
```

```
begin
    a=1'b0; b=1'b0;
#10 a=1'b0; b=1'b1;
#20 a=1'b1; b=1'b0;
#40 a=1'b1; b=1'b1;
#60 $finish;
end
endmodule
```

### 4.9 WAVEFORM:

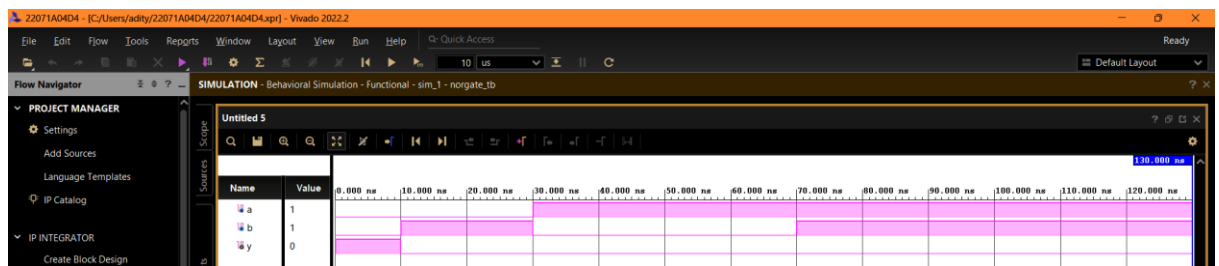

### 4.10 OBSERVATION:

Output is high for both low inputs and low for all other cases.


### 4.11 RESULT:

The Logical NOR Gate is simulated and implemented in Structural Flow Modeling.

**5.1 AIM:** To implement NOT Gate

**5.2 SOFTWARE USED:** Xilinx Vivado 2022.2

**5.3 SYMBOL:**

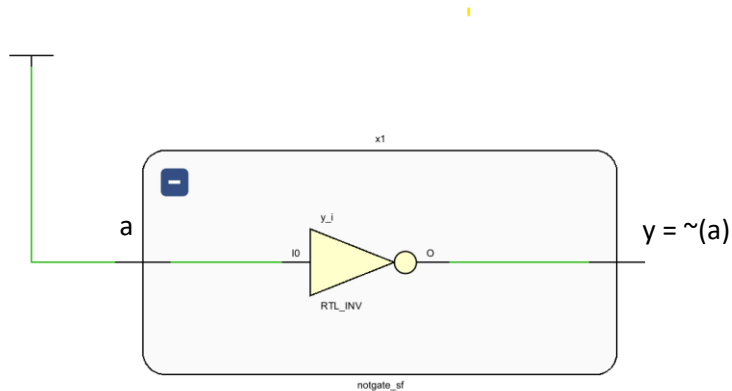

**5.4 LOGIC EXPRESSION:**

$$Y = \sim(A)$$

**5.5 BOOLEAN EXPRESSION:**

$$Y = \overline{A}$$

**5.6 TRUTH TABLE:**

INPUT	OUTPUT
A	Y
0	1
1	0

**5.7 VERILOG CODE (notgate\_sf.v):**


```
module notgate_sf(y,a);
    output y;
    input a;
    wire y;
    not (y,a);
endmodule
```

**5.8 TEST BENCH CODE (notgate\_sf\_tb.v):**

```
module notgate_sf_tb();
    reg a;
    wire y;
    notgate_sf x1(y,a);
    initial
    begin
```

```
a=1'b0; b=1'b0;  
#10 a=1'b0; b=1'b1;  
#10 $finish;  
end  
endmodule
```

### 5.9 WAVEFORM:

 

### 5.10 OBSERVATION:

Output is high for low input and low for high input.

### 5.11 RESULT:


The Logical NOT Gate is simulated and implemented in Structural Flow Modeling.



**6.1 AIM:** To implement XOR Gate

**6.2 SOFTWARE USED:** Xilinx Vivado 2022.2

**6.3 SYMBOL:**

 

**6.4 LOGIC EXPRESSION:**

$$Y = (A \oplus B)$$

**6.5 BOOLEAN EXPRESSION:**

$$Y = (\bar{A}B + A\bar{B})$$

**6.6 TRUTH TABLE:**

INPUT		OUTPUT
A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

**6.7 VERILOG CODE (xorgate\_sf.v):**

```

module xorgate_sf(y,a,b);
    output y;
    input a,b;
    wire y;
    xor (y,a,b);
endmodule

```

**6.8 TEST BENCH CODE (xorgate\_sf\_tb.v):**


```

module xorgate_sf_tb();
    reg a,b;
    wire y;

```

```
xorgate_sf x1(y,a,b);  
initial  
begin  
    a=1'b0; b=1'b0;  
    #10 a=1'b0; b=1'b1;  
    #20 a=1'b1; b=1'b0;  
    #40 a=1'b1; b=1'b1;  
    #60 $finish;  
end  
endmodule
```

### 6.9 WAVEFORM:

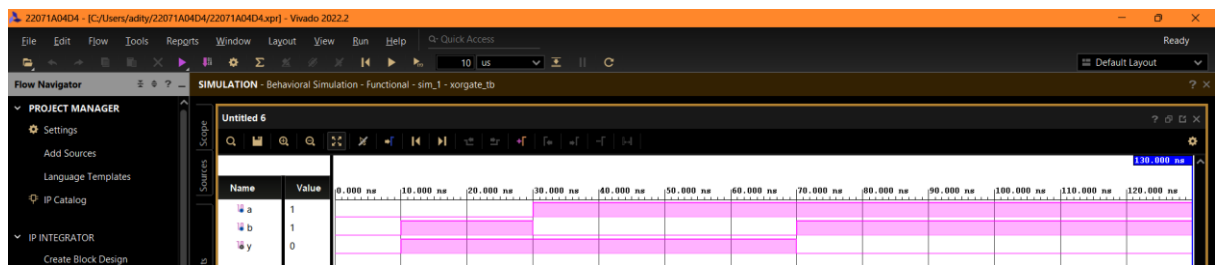

### 6.10 OBSERVATION:

Output is low for both same inputs and high for all other cases.


### 6.11 RESULT:

The Logical XOR Gate is simulated and implemented in Structural Flow Modeling.

**7.1 AIM:** To implement XNOR Gate

**7.2 SOFTWARE USED:** Xilinx Vivado 2022.2

**7.3 SYMBOL:**

 

**7.4 LOGIC EXPRESSION:**

$$Y = \sim(A \wedge B)$$

**7.5 BOOLEAN EXPRESSION:**

$$Y = (A.B + \overline{A}.\overline{B})$$

**7.6 TRUTH TABLE:**

INPUT		OUTPUT
A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

**7.7 VERILOG CODE (xnorgate\_sf.v):**

```

module xnorgate_sf(y,a,b);
    output y;
    input a,b;
    wire y;
    xnor (y,a,b);
endmodule
    
```


**7.8 TEST BENCH CODE (xnorgate\_sf\_tb.v):**

```

module xnorgate_sf_tb();
    reg a,b;
    wire y;
    xnorgate_sf x1(y,a,b);
    initial
    
```

```
begin
    a=1'b0; b=1'b0;
#10 a=1'b0; b=1'b1;
#20 a=1'b1; b=1'b0;
#40 a=1'b1; b=1'b1;
#60 $finish;
end
endmodule
```

### 7.9 WAVEFORM:

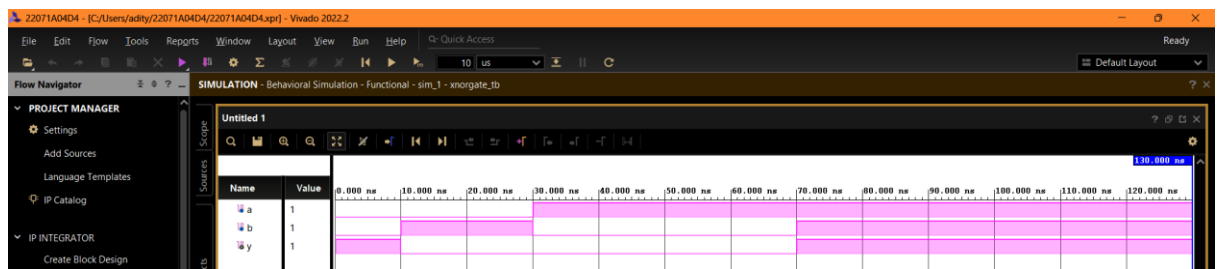

### 7.10 OBSERVATION:

Output is high for both same inputs and low for all other cases.

### 7.11 RESULT:

The Logical XNOR Gate is simulated and implemented in Structural Flow Modeling.